

# This webinar brought to you by the Relion<sup>®</sup> product family Advanced protection and control IEDs from ABB

## **Relion.** Thinking beyond the box.

Designed to seamlessly consolidate functions, Relion relays are smarter, more flexible and more adaptable. Easy to integrate and with an extensive function library, the Relion family of protection and control delivers advanced functionality and improved performance.



# ABB Protection Relay School Webinar Series

## Disclaimer

ABB is pleased to provide you with technical information regarding protective relays. The material included is not intended to be a complete presentation of all potential problems and solutions related to this topic. The content is generic and may not be applicable for circumstances or equipment at any specific facility. By participating in ABB's web-based Protective Relay School, you agree that ABB is providing this information to you on an informational basis only and makes no warranties, representations or guarantees as to the efficacy or commercial utility of the information for any specific application or purpose, and ABB is not responsible for any action taken in reliance on the information contained herein. ABB consultants and service representatives are available to study specific operations and make recommendations on improving safety, efficiency and profitability. Contact an ABB sales representative for further information.

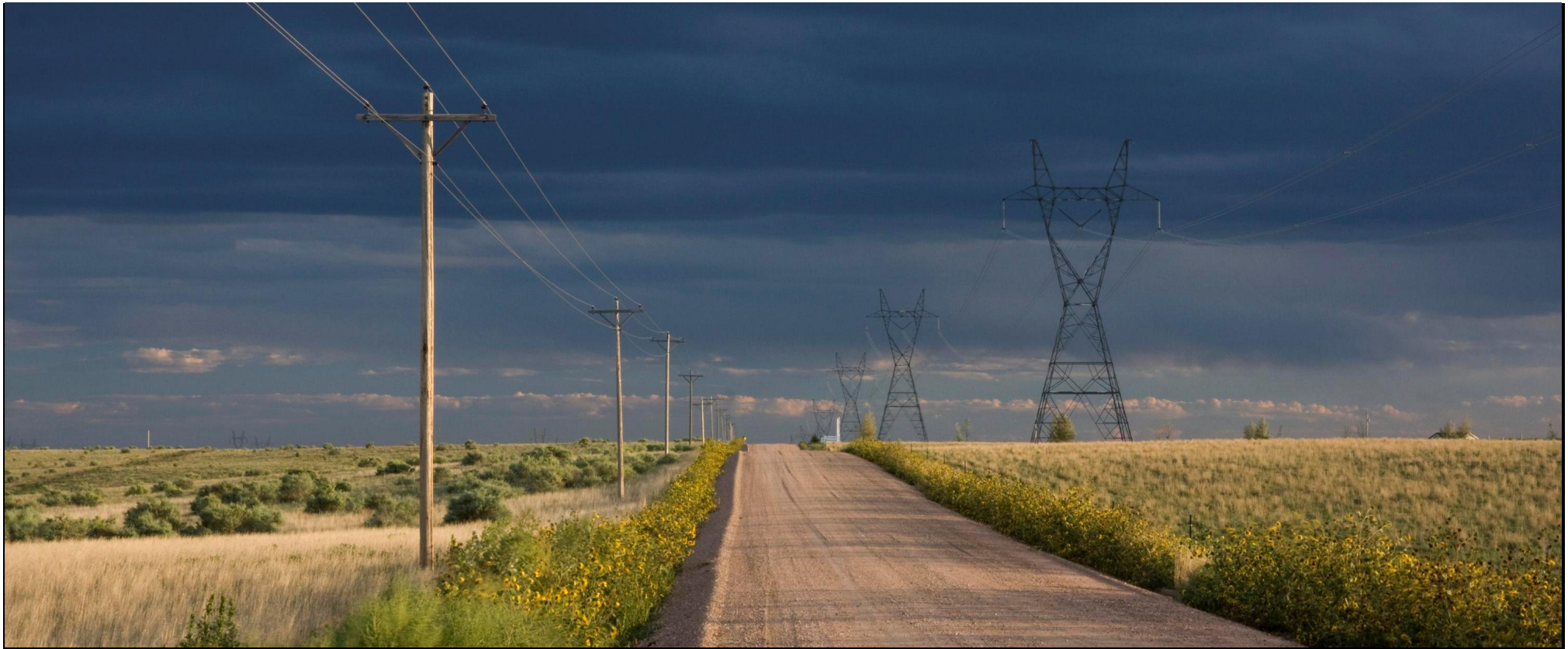


ABB Protective Relay School Webinar Series, Michael Fleck, July 9, 2013

# Symmetrical Components Examples & Application

## Power System Fundamentals

# Profile

## Michael Fleck, P.E.



- Regional Technical Manager, Midwest USA
- BSEE, Rose-Hulman Inst. of Technology, Indiana
- MSEE, Arizona State University, Arizona
- Professional Engineer (P.E.), Indiana
- IEEE – Power & Energy Society Member
- Experiences:
  - ✓ ABB DA Regional Technical Manager, configuration of products to meet customer applications, customer training
  - ✓ Protection and Control Engineer, system modeling, control design, mentoring junior engineers for national consulting company,
  - ✓ Transmission and Distribution P&C engineer, system modelling, system study, design, relay setting, trouble shooting for utility company

# Learning Objectives

- What we will discuss
  - Overview of converting phase quantities to symmetrical quantities and symmetrical to phase
  - Sequence Impedance networks – How do we build one?
  - Evaluating a Impedance network – Example Problem
  - Insights into the Example Problem
- Why do we use this method?
  - Not using it would require writing loop equations for the system and solving. – For simple systems it's not an easy task
  - To date it is still the only real practical solution to problems of unbalanced electrical circuits.

# Symmetrical Components

- The method of symmetrical components was discovered by **Dr Charles Fortescue** while investigating problems of a single phase railway system.
- Introduced in 1918 in a classic AIEE transaction “Method of Symmetrical Co-ordinates Applied to Solution of Polyphase Networks”.
- The application to the analysis and operation of three phase power systems was broadened by **C. F. Wagner, R. D. Evans** through a series of articles they published in the Westinghouse magazine “*The Electric Journal*” that ran from March 1928 through November 1931

# Symmetrical Components

- Symmetrical Components is often referred to as the language of the Relay Engineer but it is important for all engineers that are involved in power.
- The terminology is used extensively in the power engineering field and it is important to understand the basic concepts and terminology.
- Used to be more important as a calculating technique before the advanced computer age.
- Is still useful and important to make sanity checks and back-of-an-envelope calculation.





# Symmetrical components and fault analysis

## Voltage & Current Conversion Review




# Symmetrical Components

- Balanced load supplied by balanced voltage results in balanced current.
  - i. This situation results in only positive sequence components
  - ii. Seldom achievable in real world applications
- Positive Sequence currents produce only positive sequence voltages, Negative sequence currents produce only negative sequence voltages, and zero sequence currents produce only zero sequence voltages
- For unbalanced systems: Positive Sequence currents produce positive, negative and sometimes zero sequence voltages, Negative sequence currents produce positive, negative and sometimes zero sequence voltages, and zero sequence currents produce positive, negative, and zero sequence voltages

# Symmetrical Components

- For the General Case of 3 unbalanced voltages



- 6 degrees of freedom

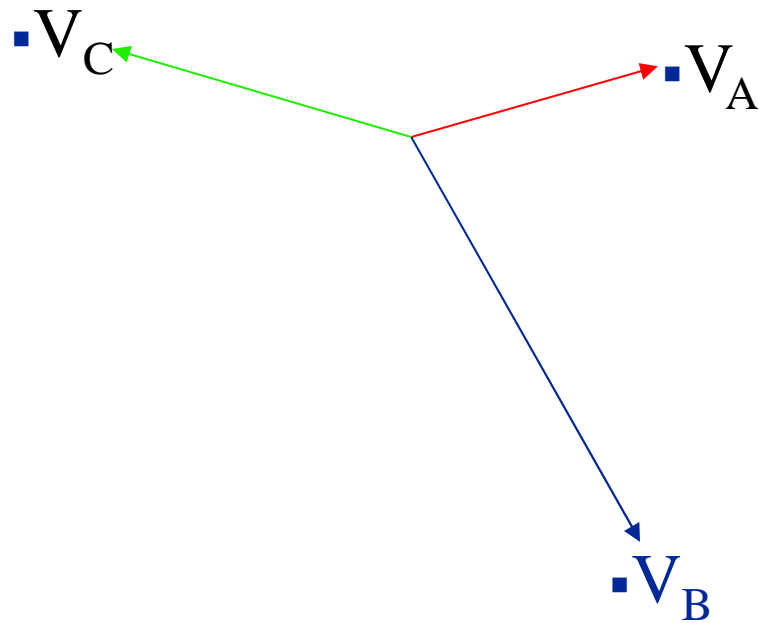

- Can define 3 sets of voltages designated as positive sequence, negative sequence and zero sequence

# Symmetrical Components Positive Sequence

▪ **2 degrees of freedom**

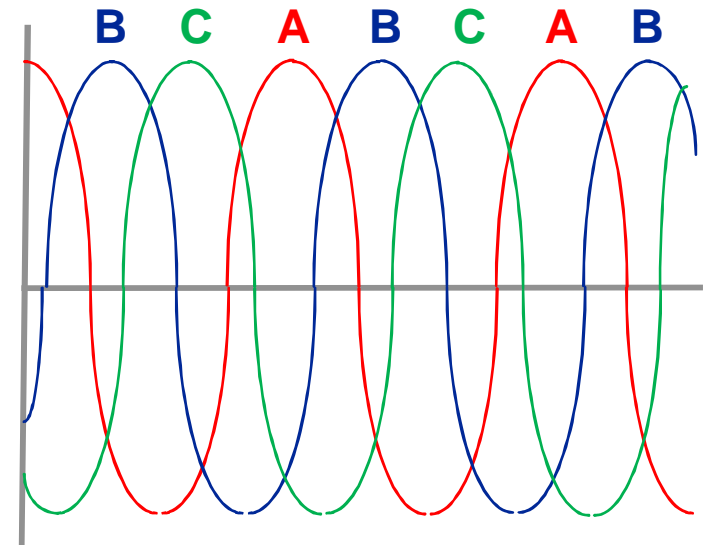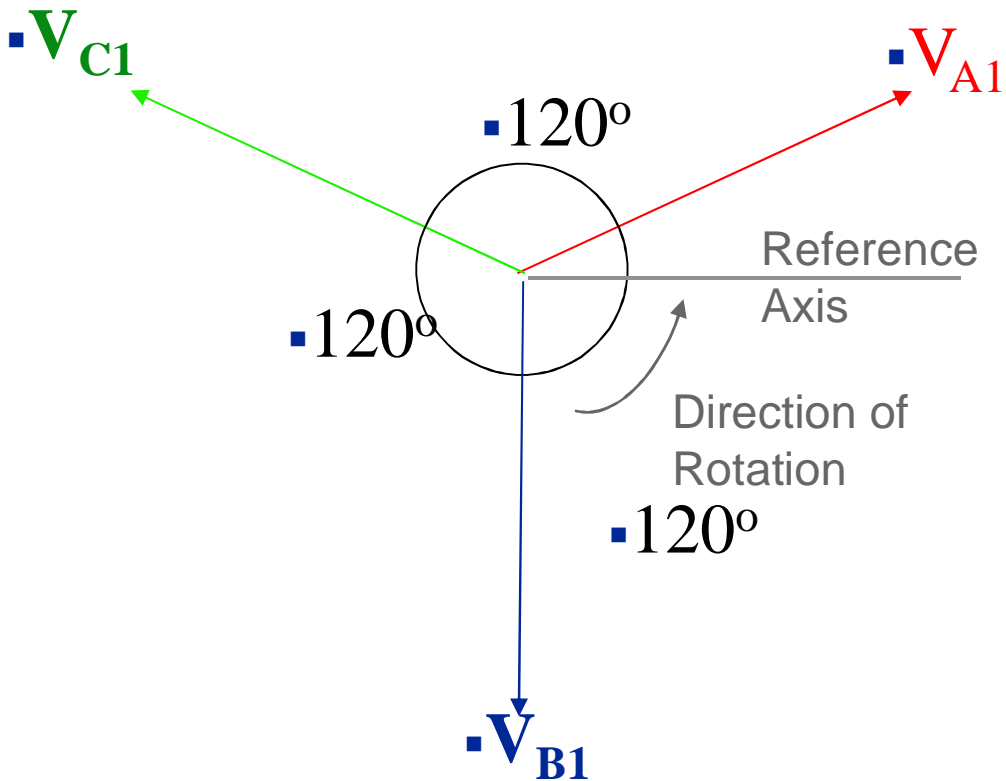

▪  $V_{A1} = V_{A1}$



▪  $V_{B1} = a^2 V_{A1}$

▪  $V_{C1} = a V_{A1}$

▪ **a is operator 1/120°**

# Symmetrical Components Negative Sequence

▪ **2 degrees of freedom**

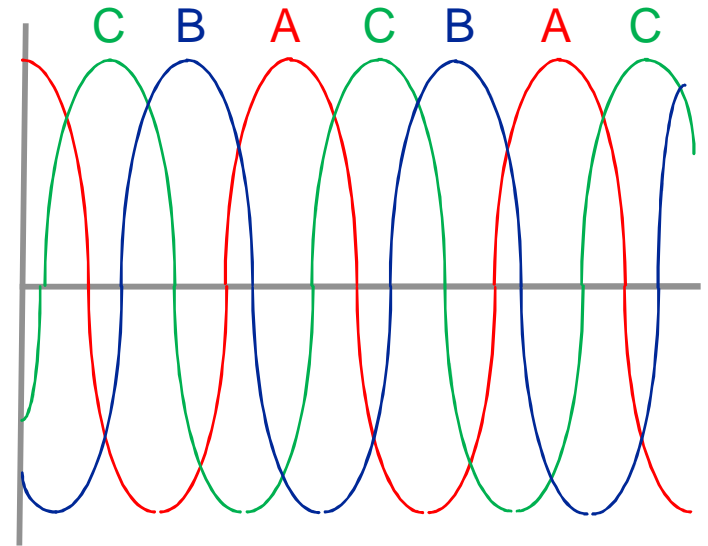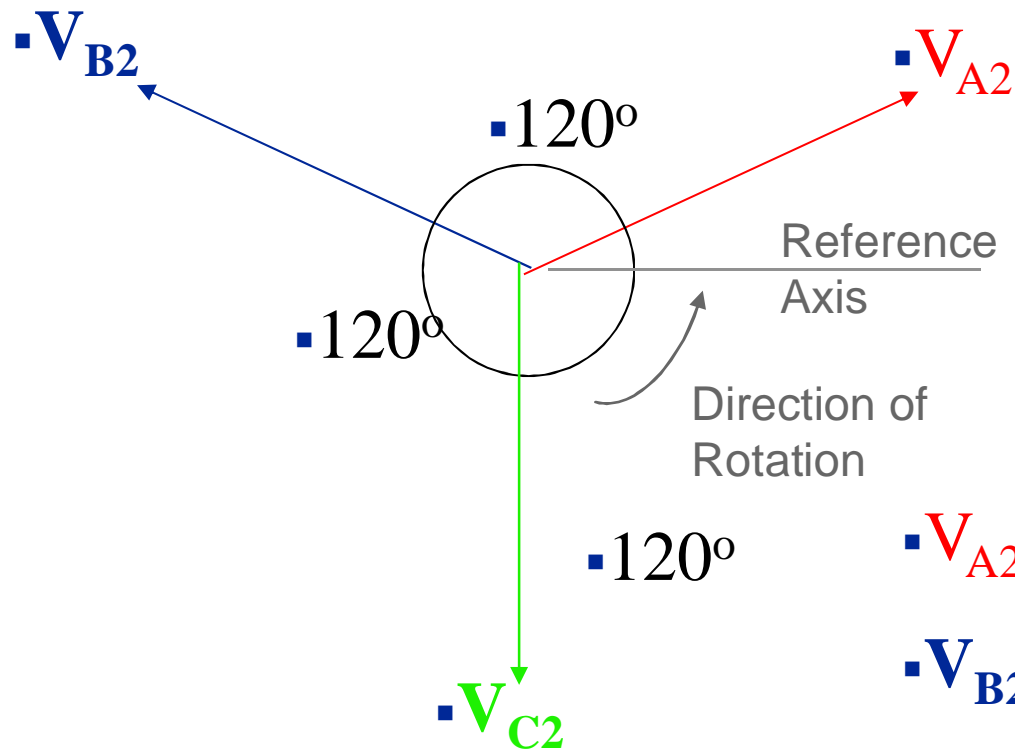

$$\cdot V_{A2} = V_{A2}$$


$$\cdot V_{B2} = a V_{A2}$$

$$\cdot V_{C2} = a^2 V_{A2}$$


▪ **a is operator  $\frac{1}{120^\circ}$**

# Symmetrical Components Zero Sequence

- 2 degrees of freedom

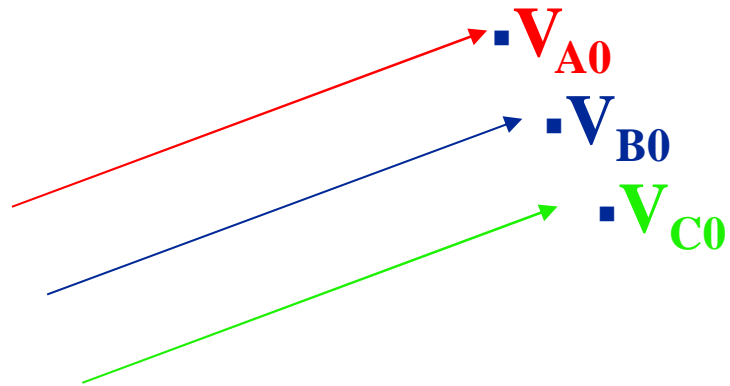

$$\cdot V_{A0} = V_{B0} = V_{C0}$$

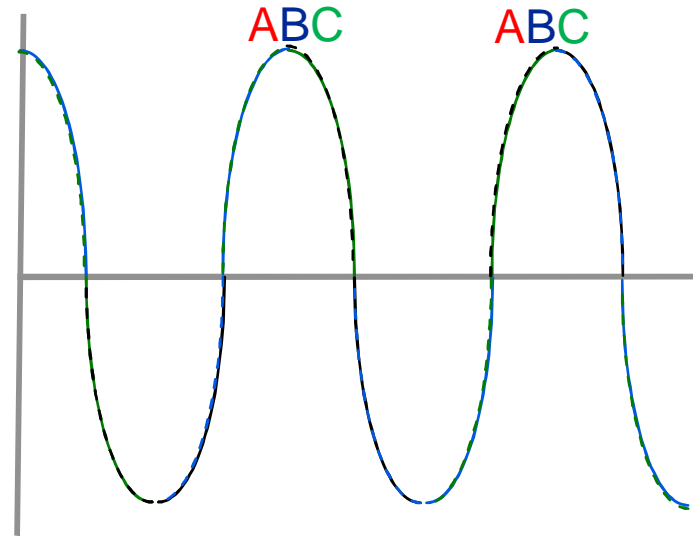



# Symmetrical Components

- **Reforming the phase voltages in terms of the symmetrical component voltages:**

$$V_A = V_{A0} + V_{A1} + V_{A2}$$

$$V_B = V_{B0} + V_{B1} + V_{B2}$$

$$V_C = V_{C0} + V_{C1} + V_{C2}$$

- **What have we gained? We started with 3 phase voltages and now have 9 sequence voltages. The answer is that the 9 sequence voltages are not independent and can be defined in terms of other voltages.**

# Symmetrical Components

**Rewriting the sequence voltages in term of the Phase A sequence voltages:**

$$\begin{array}{l} \mathbf{V}_A = \mathbf{V}_{A0} + \mathbf{V}_{A1} + \mathbf{V}_{A2} \\ \mathbf{V}_B = \mathbf{V}_{A0} + \mathbf{a}^2 \mathbf{V}_{A1} + \mathbf{a} \mathbf{V}_{A2} \\ \mathbf{V}_C = \mathbf{V}_{A0} + \mathbf{a} \mathbf{V}_{A1} + \mathbf{a}^2 \mathbf{V}_{A2} \end{array} \quad \xrightarrow{\text{Drop A}} \quad \begin{array}{l} \mathbf{V}_A = \mathbf{V}_0 + \mathbf{V}_1 + \mathbf{V}_2 \\ \mathbf{V}_B = \mathbf{V}_0 + \mathbf{a}^2 \mathbf{V}_1 + \mathbf{a} \mathbf{V}_2 \\ \mathbf{V}_C = \mathbf{V}_0 + \mathbf{a} \mathbf{V}_1 + \mathbf{a}^2 \mathbf{V}_2 \end{array}$$

**Suggests matrix notation:**

$$\begin{bmatrix} \mathbf{V}_A \\ \mathbf{V}_B \\ \mathbf{V}_C \end{bmatrix} = \begin{bmatrix} \mathbf{1} & \mathbf{1} & \mathbf{1} \\ \mathbf{1} & \mathbf{a}^2 & \mathbf{a} \\ \mathbf{1} & \mathbf{a} & \mathbf{a}^2 \end{bmatrix} \begin{bmatrix} \mathbf{V}_0 \\ \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

$[\mathbf{V}_P] = [\mathbf{A}] [\mathbf{V}_S]$

# Symmetrical Components

**[V<sub>P</sub>] = Phase Voltages**

**[V<sub>S</sub>] = Sequence Voltages**

$$[\mathbf{A}] = \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \quad [\mathbf{V}_P] = [\mathbf{A}][\mathbf{V}_S]$$

**Pre-multiplying by [A]<sup>-1</sup>**

$$[\mathbf{A}]^{-1}[\mathbf{V}_P] = [\mathbf{A}]^{-1}[\mathbf{A}][\mathbf{V}_S] = [\mathbf{I}][\mathbf{V}_S]$$

$$[\mathbf{V}_S] = [\mathbf{A}]^{-1} [\mathbf{V}_P]$$

$$[\mathbf{A}]^{-1} = 1/3 \begin{pmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{pmatrix} \quad [\mathbf{V}_S] = [\mathbf{A}]^{-1}[\mathbf{V}_P]$$



# Symmetrical components & Fault Analysis Impedance Networks


# Symmetrical Components

Typical System Parameter used in Symmetrical Component Analysis

- Transmission Lines
- Transformers
- Generators


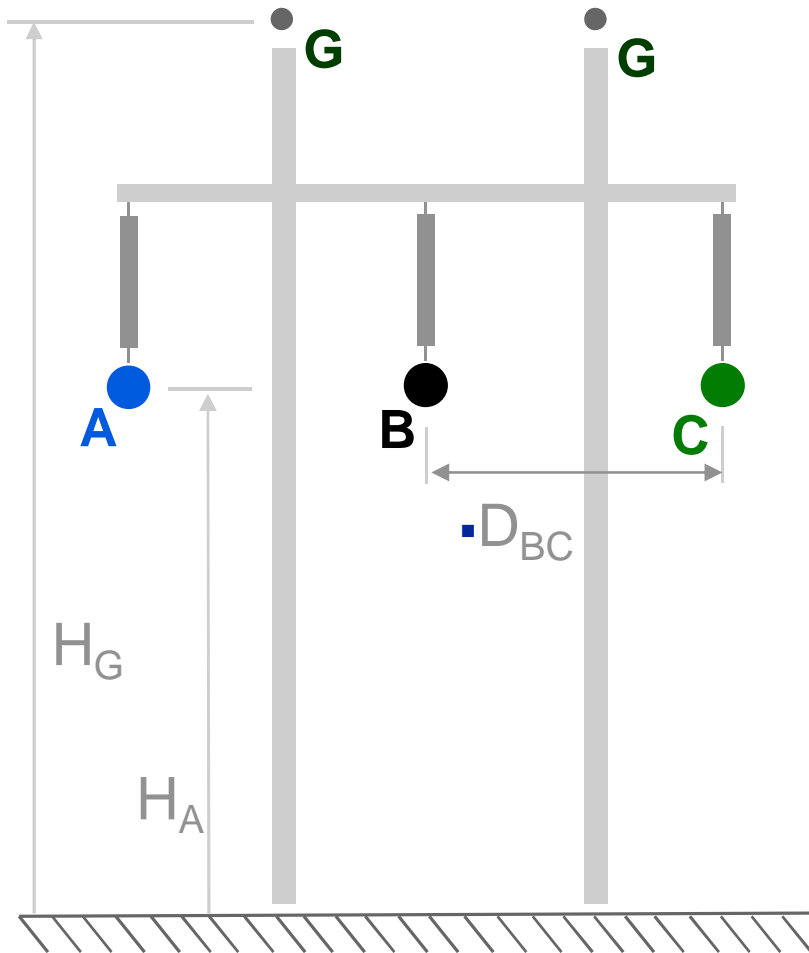
# Symmetrical Components – Line Constants




## Transmission Line Impedance

- Size and type of phase and ground conductors
- Geometric configuration of the transmission line
- Transpositions over the length of the line
- Shunt capacitance is generally neglected for fault studies


# Transmission Line Models

The general models for transmission lines

## Positive and Negative Sequence

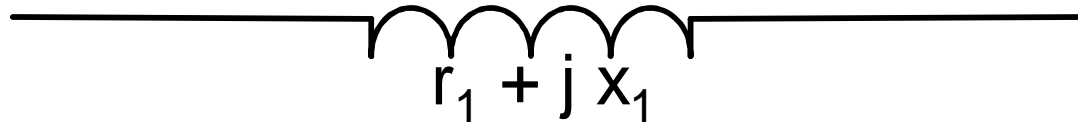

## • Zero Sequence

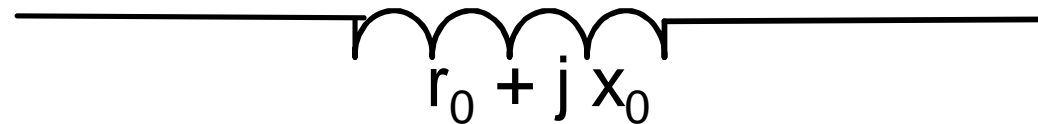

# Transmission Line Models

## Positive & Negative Sequence ( $Z_1 = Z_2$ )

- $Z_1 = R_1 + jX_1$
- $R_1 = r/n$  for n conductors per phase:
- r can be found in lookup tables showing cable resistance

**Note skin effect:  $r_{dc} < r_{60Hz}$**


- $X_1$  can be found from the general equation for inductance

$$L_1 = 2 \times 10^{-7} \ln \frac{D_{EQ}}{D_{SL}} \text{ Henries/meter}$$
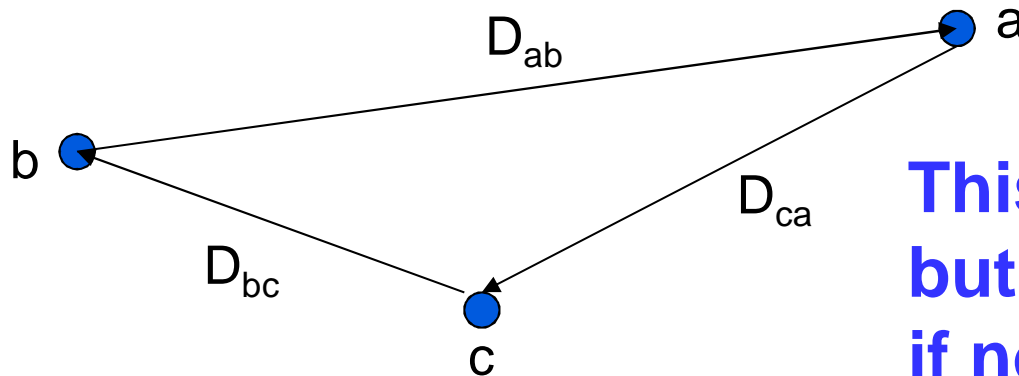
# Transmission Line Models

$$X_1 = 2\pi f L_1 = .1213 \ln \frac{D_{EQ}}{D_{SL}} \quad \Omega \text{ per mile for 60 Hz}$$

$$D_{EQ} = (D_{ab} \times D_{bc} \times D_{ca})^{\frac{1}{3}}$$



**This assumes transposition but is reasonably accurate if not transposed.**




# Transmission Line Models

## How to calculate $D_{SL}$

If there are  $n$  conductors per phase,  $D_{SL}$  is the distance from every conductor in the bundle to every other conductor to the  $1/n^2$

• For 3 conductor bundle  $D_{SL} = [(d)(d)(gmr)(d)(gmr)(d)(gmr)(d)(d)]^{1/9}$

$$D_{SL} = [(gmr)d^2]^{1/3}$$

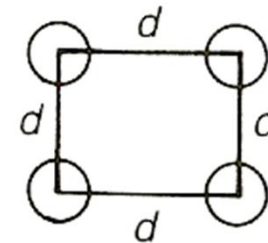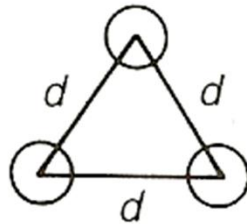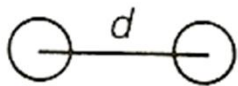

**For a 1-conductor bundle:**  $D_{SL} = gmr$

**For a 2-conductor bundle:**  $D_{SL} = \sqrt{gmr \times d}$

**For a 3-conductor bundle:**  $D_{SL} = \sqrt[3]{gmr \times d^2}$

**For a 4-conductor bundle:**  $D_{SL} = 1.091 \times \sqrt[4]{gmr \times d^3}$



# Transmission Line Models

## Example:


Find the positive sequence model for 20 mile of transmission line with 2-conductor bundle 2156 KCM ACSR Conductors (Bluebird) and the following conductor configuration:

Found from cable lookup table:

Diameter = 1.762 in. Radius = 0.881 in. = 0.0734 ft.

gmr = 0.0586 ft. Resistance = 0.0515  $\Omega$ /mile

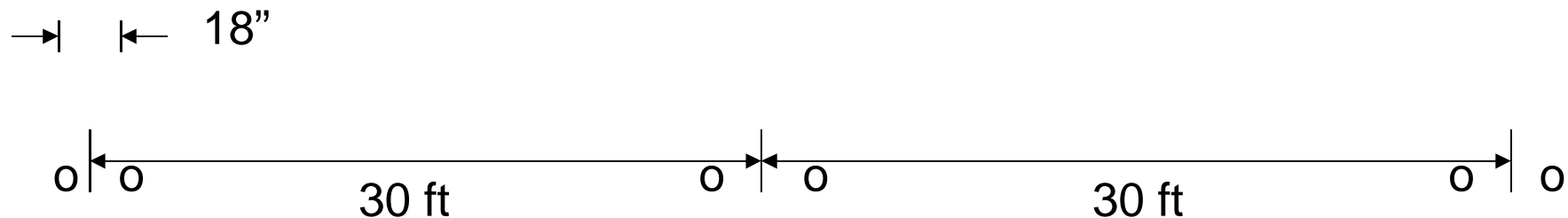**Find:** Positive and Negative Sequence Impedance for a 20 mile line



# Transmission Line Models

Code word	Aluminum area, cmil	Stranding Al/St	Layers of aluminum	Outside diameter, in	Resistance			GMR $\approx \sqrt{r}$ $D_s$ , ft	Reactance
					Dc, 20°C, $\Omega/1,000$ ft	Ac, 60 Hz			Inductive $X_a$ , $\Omega/\text{mi}$
						20°C, $\Omega/\text{mi}$	50°C, $\Omega/\text{mi}$		
Waxwing	266,800	18/1	2	0.609	0.0646	0.3488	0.3831	0.0198	0.476
Partridge	266,800	26/7	2	0.642	0.0640	0.3452	0.3792	0.0217	0.465
Ostrich	300,000	26/7	2	0.680	0.0569	0.3070	0.3372	0.0229	0.458
Merlin	336,400	18/1	2	0.684	0.0512	0.2767	0.3037	0.0222	0.462
Linnet	336,400	26/7	2	0.721	0.0507	0.2737	0.3006	0.0243	0.451
Triole	336,400	30/7	2	0.741	0.0504	0.2719	0.2987	0.0255	0.445
Chickadee	397,500	18/1	2	0.743	0.0433	0.2342	0.2572	0.0241	0.452
Wisp	397,500	26/7	2	0.783	0.0430	0.2323	0.2551	0.0264	0.441
Pelican	477,000	18/1	2	0.814	0.0361	0.1957	0.2148	0.0264	0.441
Nicker	477,000	24/7	2	0.846	0.0359	0.1943	0.2134	0.0284	0.432
Fawk	477,000	26/7	2	0.858	0.0357	0.1931	0.2120	0.0289	0.430
Wren	477,000	30/7	2	0.883	0.0355	0.1919	0.2107	0.0304	0.424
Sprey	556,500	18/1	2	0.879	0.0309	0.1679	0.1843	0.0284	0.432
Parakeet	556,500	24/7	2	0.914	0.0308	0.1669	0.1832	0.0306	0.423
Wove	556,500	26/7	2	0.927	0.0307	0.1663	0.1826	0.0314	0.420
Wook	636,000	24/7	2	0.977	0.0269	0.1461	0.1603	0.0327	0.415
Wrosbank	636,000	26/7	2	0.990	0.0268	0.1454	0.1596	0.0335	0.412
Wrake	795,000	26/7	2	1.108	0.0215	0.1172	0.1284	0.0373	0.399
Wern	795,000	45/7	3	1.063	0.0217	0.1188	0.1302	0.0352	0.406
Wail	954,000	45/7	3	1.185	0.0181	0.0997	0.1092	0.0386	0.395
Wardinal	954,000	54/7	3	1.196	0.0180	0.0988	0.1082	0.0402	0.390
Wrtolan	1,033,500	45/7	3	1.213	0.0167	0.0924	0.1011	0.0402	0.390
Wuejay	1,113,000	45/7	3	1.259	0.0155	0.0861	0.0941	0.0415	0.386
Winch	1,113,000	54/19	3	1.293	0.0155	0.0856	0.0937	0.0436	0.380
Wittern	1,272,000	45/7	3	1.345	0.0136	0.0762	0.0832	0.0444	0.378
Wessant	1,272,000	54/19	3	1.382	0.0135	0.0751	0.0821	0.0466	0.372
Wobolink	1,431,000	45/7	3	1.427	0.0121	0.0684	0.0746	0.0470	0.371
Wlover	1,431,000	54/19	3	1.465	0.0120	0.0673	0.0735	0.0494	0.365
Wapwing	1,590,000	45/7	3	1.502	0.0109	0.0623	0.0678	0.0498	0.364
Walcon	1,590,000	54/19	3	1.545	0.0108	0.0612	0.0667	0.0523	0.358
Wuebird	2,156,000	84/19	4	1.762	0.0080	0.0476	0.0515	0.0586	0.344



# Transmission Line Example

Diameter = 1.762 in. Radius = 0.881 in. = 0.0734 ft.

gmr = 0.0586 ft. Resistance = 0.0515  $\Omega$ /mile

$$r_1 = \frac{.0515}{2} = .0258 \Omega / mi$$

$$D_{eq} = [(30)(30)(60)]^{1/3} = (54,000)^{1/3} = 37.8 ft.$$

$$D_{sL} = [(1.5)(.0586)]^{1/2} = 0.296 ft.$$

$$x_1 = .1213 \ln \frac{37.8}{.296} \Omega / mi$$

# Transmission Line Example

$$Z_1 = Z_2 = (r_1 + x_1) \text{Line}_{length}$$

$$Z_1 = Z_2 = 0.52 + j11.8\Omega = 11.81\angle 87.57^\circ$$


$$11.81\angle 87.57^\circ$$



# Transmission Line Models Z0

- If  $I_a + I_b + I_c \neq 0$  there will be neutral current flow
- If the neutral is grounded all of part of the neutral current will flow in the ground
- Need to determine the impedance to the flow of this current:  $Z_0$
- Made possible by Carson's work which shows that earth can be modeled by one or more equivalent conductors
- We will use one equivalent conductor below the earth's surface for each real conductor.

# Transmission Line Models Z0

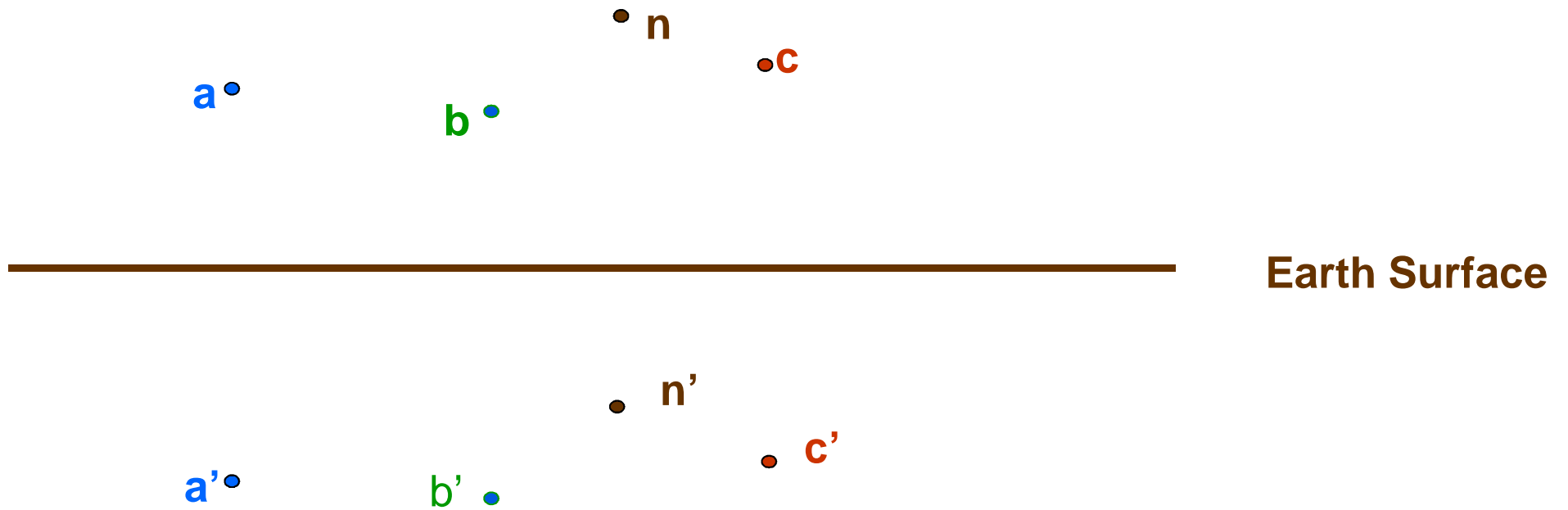

**Just one OHGW to simplify work but showing principal**

# Transmission Line Models Z0 – Carson's Formula

$D_{k'k'} = D_{kk} = \text{gmr of the overhead conductor}$

$$D_{kk'} = 658.5 \sqrt{\frac{\rho}{f}} \text{ Meters}$$

$\rho = \text{earth resistivity in ohm-meters}$

$$R_{k'} = 9.869 * 10^{-7} f \text{ Ohms / meter}$$

where:  $f = \text{frequency in Hz}$

# Transmission Line Models – Z<sub>0</sub>

Z<sub>0</sub> is much more difficult to find and depend on:

- Ground resistance
- Conductor height above ground
- Distance from phase conductors to overhead ground wires (OHGW)
- Characteristics of OHGW
- Z<sub>0</sub> > Z<sub>1</sub> due to mutual coupling between phases. Mutual coupling to adjacent circuits must be considered
- Rule of Thumb:  $2Z_1 < Z_0 < 4Z_1$



# Transformer Constants

- Factors to Consider
  - Polarity
  - Three Phase Connections
  - Number of Windings
  - Core Design

# Transformer Models

The general models for transformer lines

$$jX_1 = jX_2 = jX_0$$

The one exception to this is when we have a three phase core-type transformer


## Positive and Negative Sequence Connections



## Zero Sequence

Dependant on Transformer winding connections

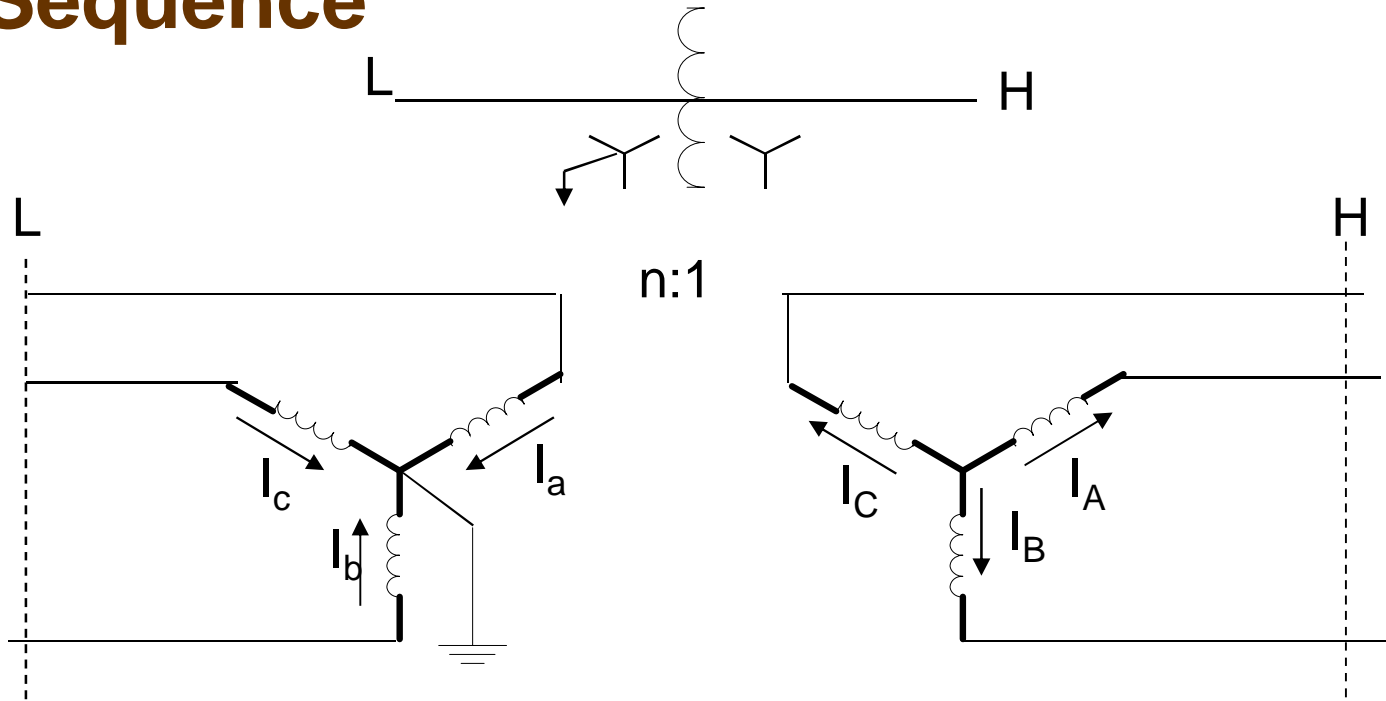
# Transformer Connections for Zero Sequence



$I_a + I_b + I_c$  is not necessarily 0 if we only look at Low Voltage circuit


But we know  $I_L = nI_H$  :  $I_a = nI_A$   $I_b = nI_B$  and  $I_c = nI_C$

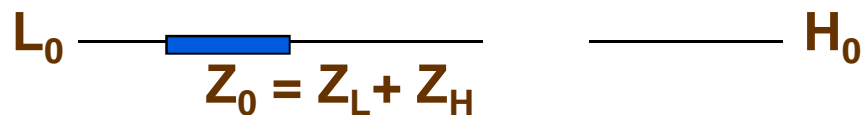Since  $I_A + I_B + I_C = 0$  ,  $I_a + I_b + I_c = 0$  and  $I_0 = 0$



No zero sequence current flow through transformer

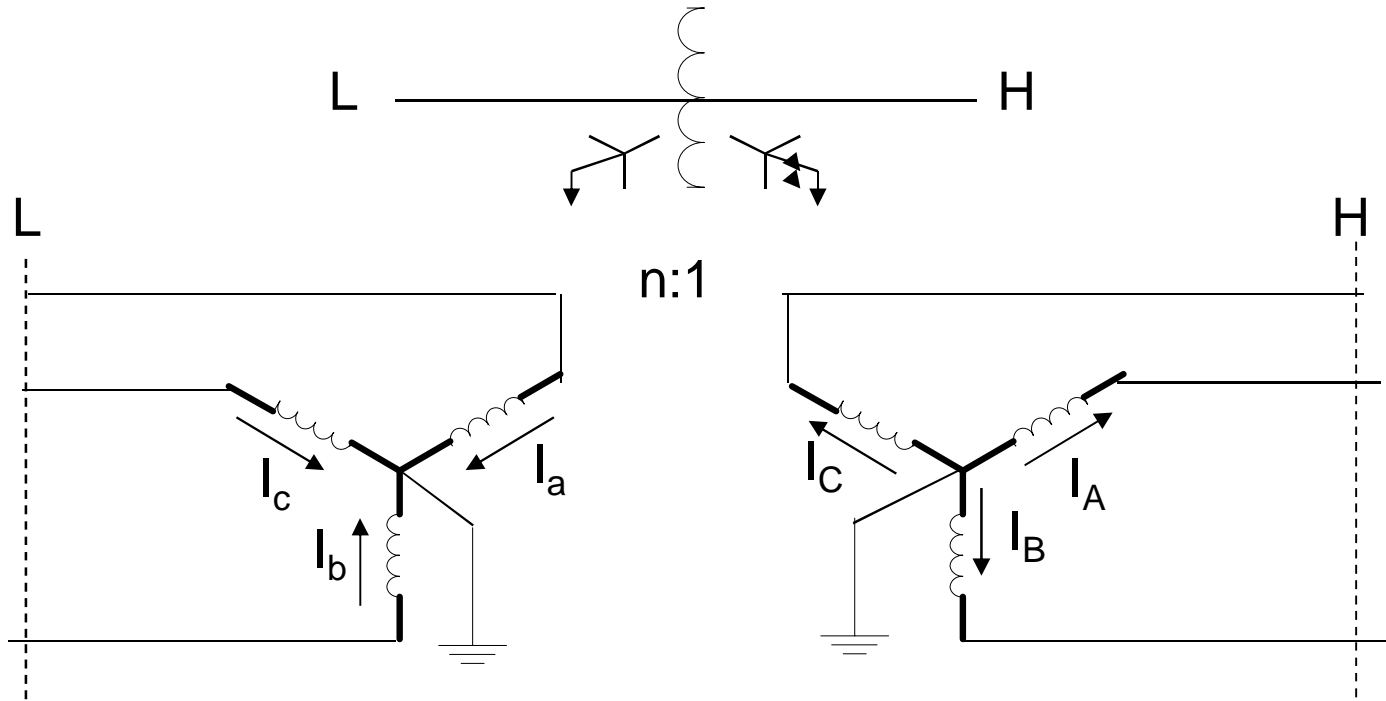
# Transformer Connections for Zero Sequence




$I_a + I_b + I_c$  is not necessarily 0 and  $I_A + I_B + I_C$  is not necessarily.

Therefore  $I_0$  is not necessarily 0,

$I_0$  can flow through the transformer.

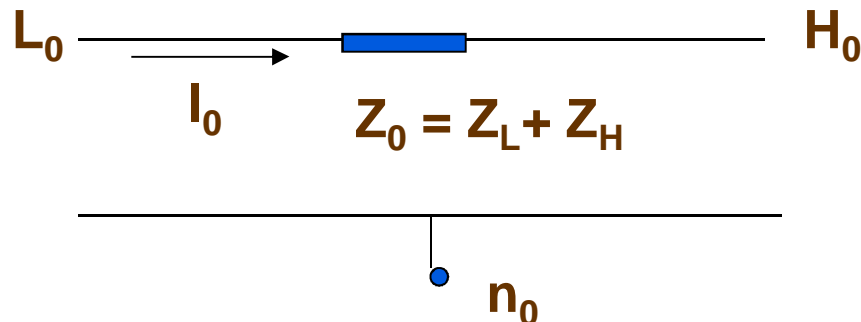

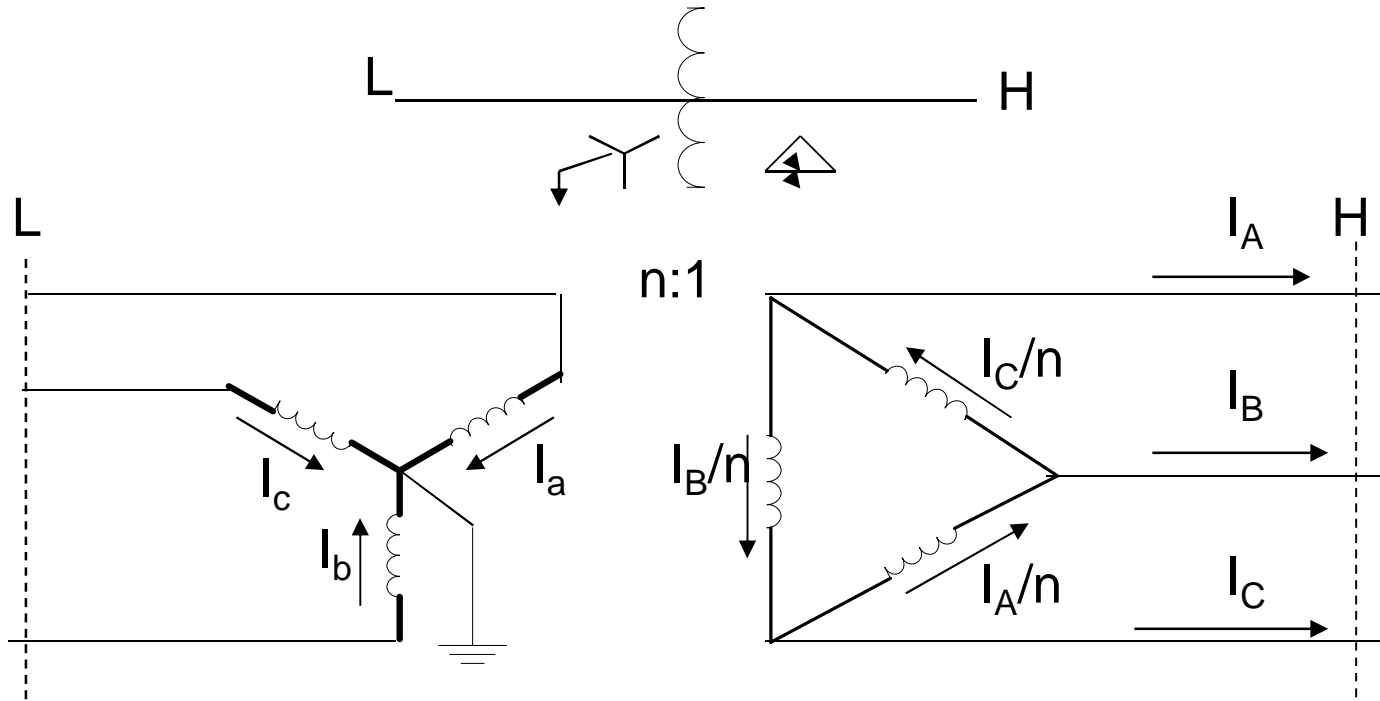
# Transformer Connections for Zero Sequence




$I_a + I_b + I_c$  is not necessarily 0 and  $I_A/n + I_B/n + I_C/n$  is not necessarily 0

But  $I_A + I_B + I_C = 0$

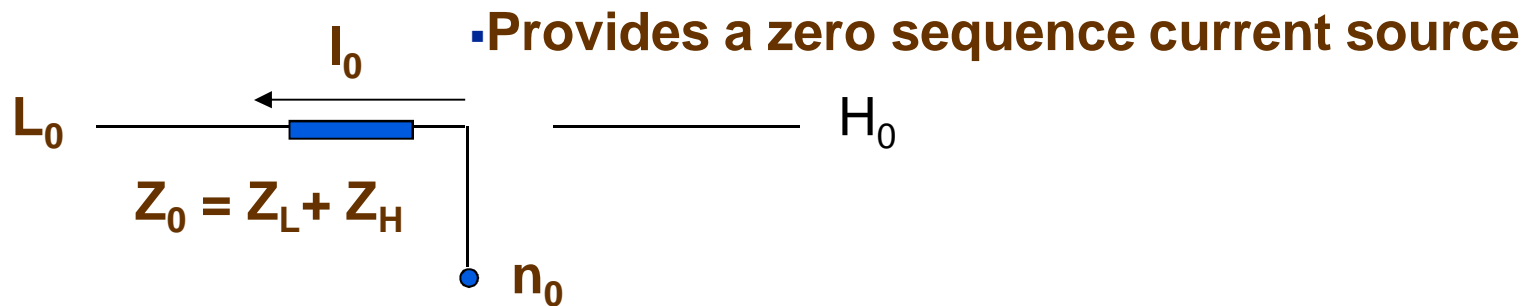

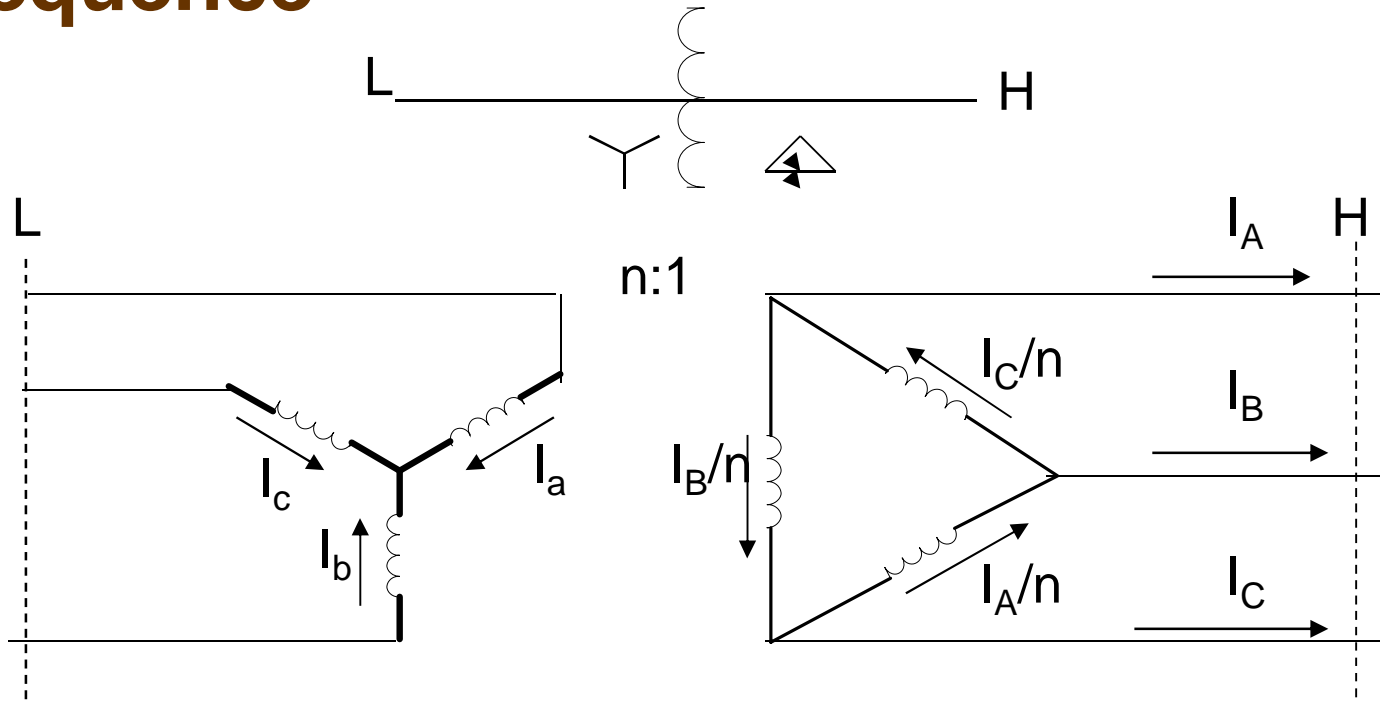
# Transformer Connections for Zero Sequence




$I_a + I_b + I_c = 0$     $I_A/n + I_B/n + I_C/n$  is not necessarily 0, but  $I_A + I_B + I_C = 0$


- No zero sequence current flow

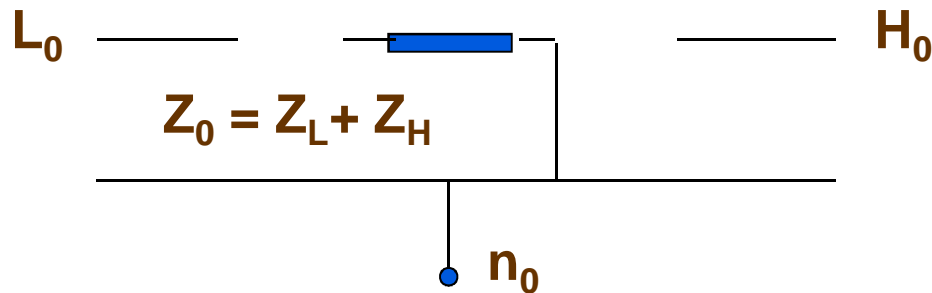

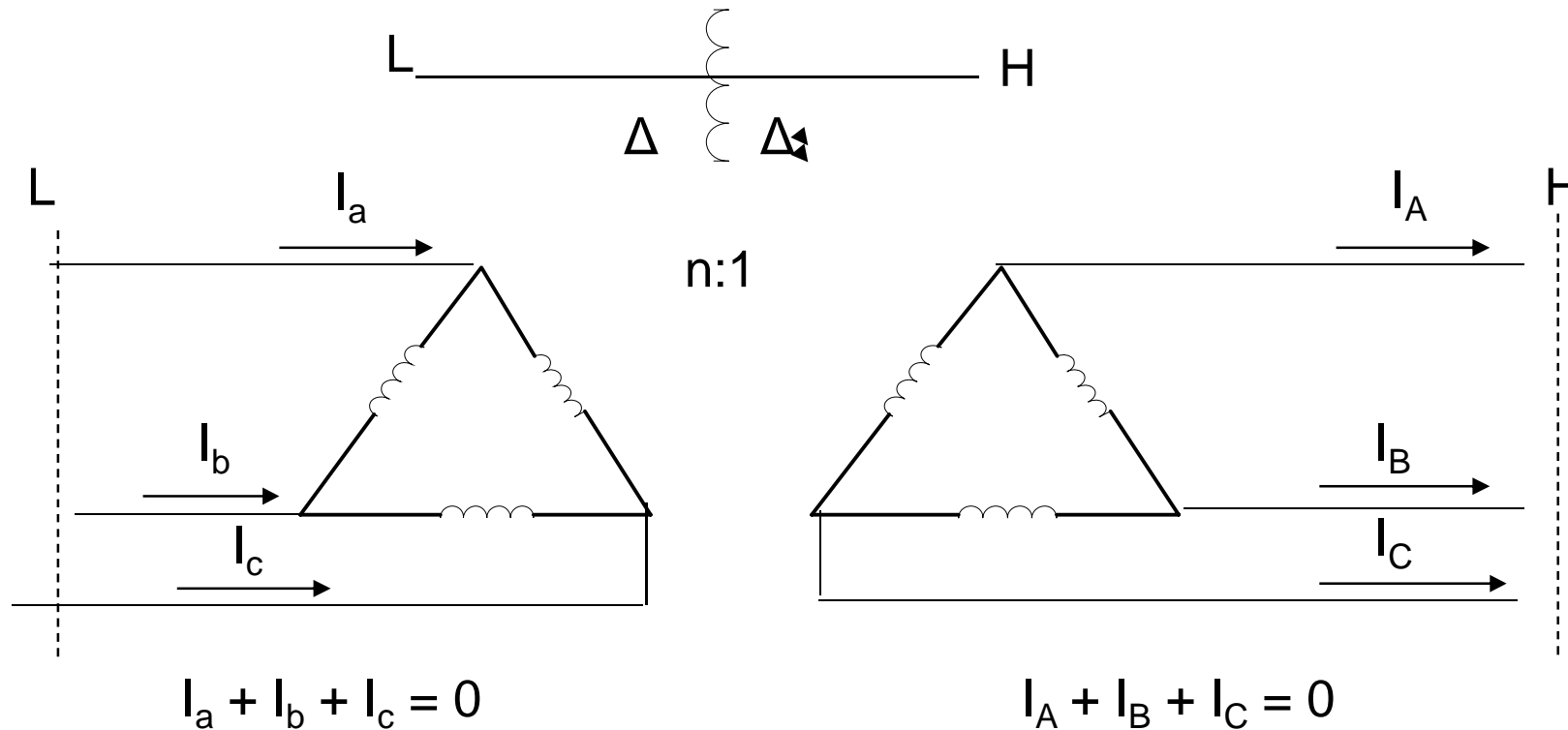
# Transformer Connections for Zero Sequence



**No zero sequence current flow**

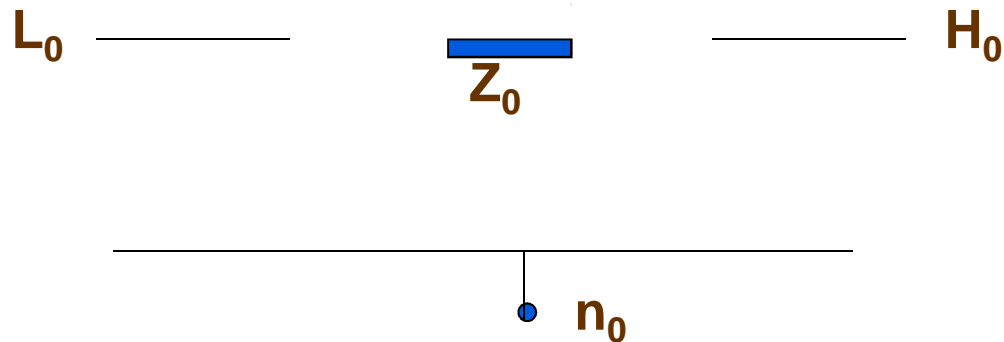

# Rotating Machine Sequence Networks

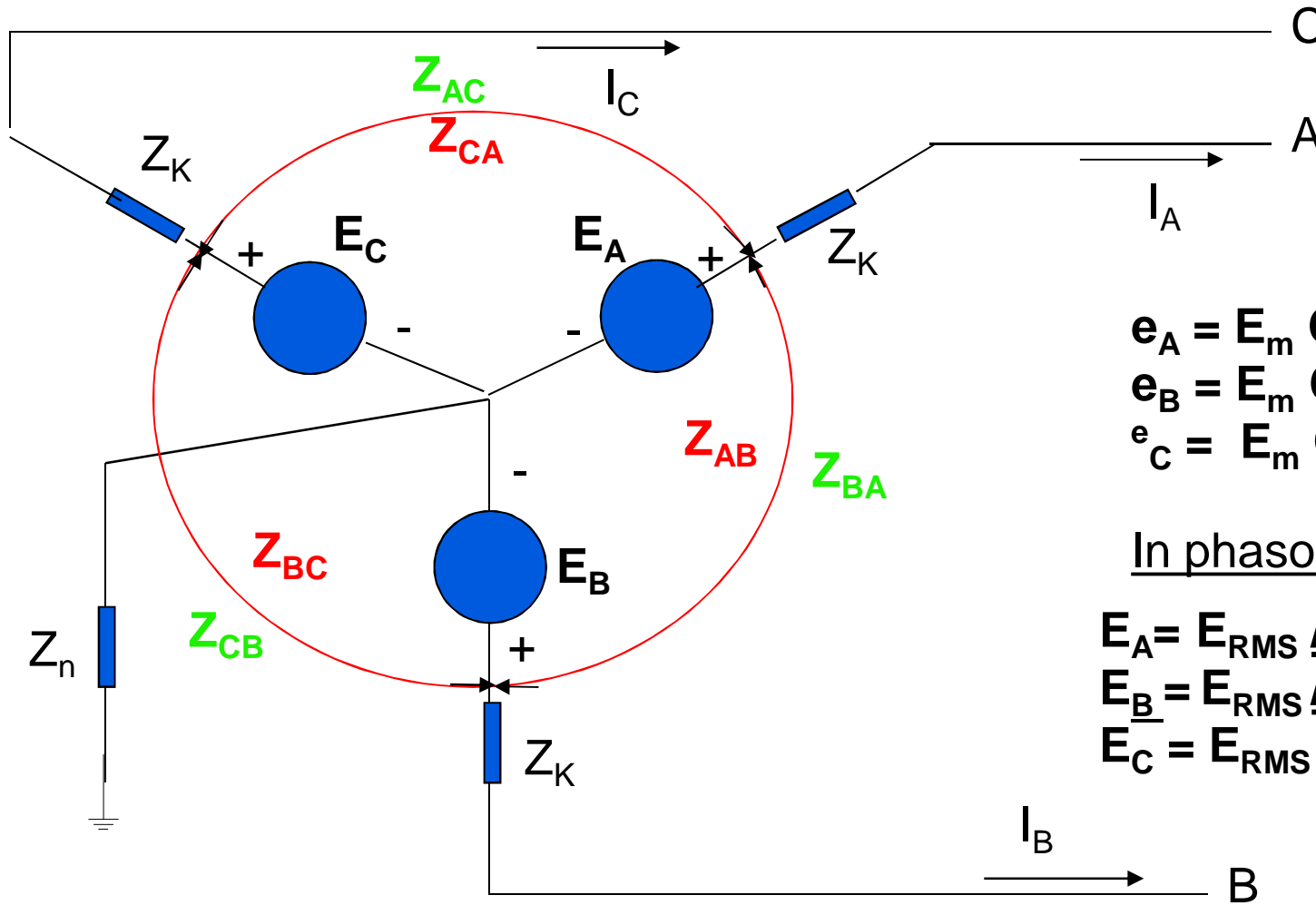

$$e_A = E_m \cos \omega t$$

$$e_B = E_m \cos(\omega t - 120^\circ)$$

$$e_C = E_m \cos(\omega t + 120^\circ)$$

In phasor form:

$$E_A = E_{RMS} \underline{/0} = E$$

$$E_B = E_{RMS} \underline{/ -120^\circ} = a^2 E$$

$$E_C = E_{RMS} \underline{/120^\circ} = a E$$



# Rotating Machine Sequence Networks


$$\begin{aligned}
 E_A &= E_{\text{RMS}} / 0 = E \\
 E_B &= E_{\text{RMS}} / -120^\circ = a^2 E \\
 E_C &= E_{\text{RMS}} / 120^\circ = a E
 \end{aligned}
 \quad \text{or} \quad
 [E_{Pg}] = \begin{bmatrix} E \\ a^2 E \\ aE \end{bmatrix}
 \begin{matrix} a \\ b \\ c \end{matrix}$$

$$[E_{Sg}] = [A]^{-1} [E_{Pg}] = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} E \\ a^2 E \\ aE \end{bmatrix} = \begin{bmatrix} 0 \\ E \\ 0 \end{bmatrix}
 \begin{matrix} 0 \\ 1 \\ 2 \end{matrix}$$

- Therefore, only the **positive** sequence system has a generator voltage source.

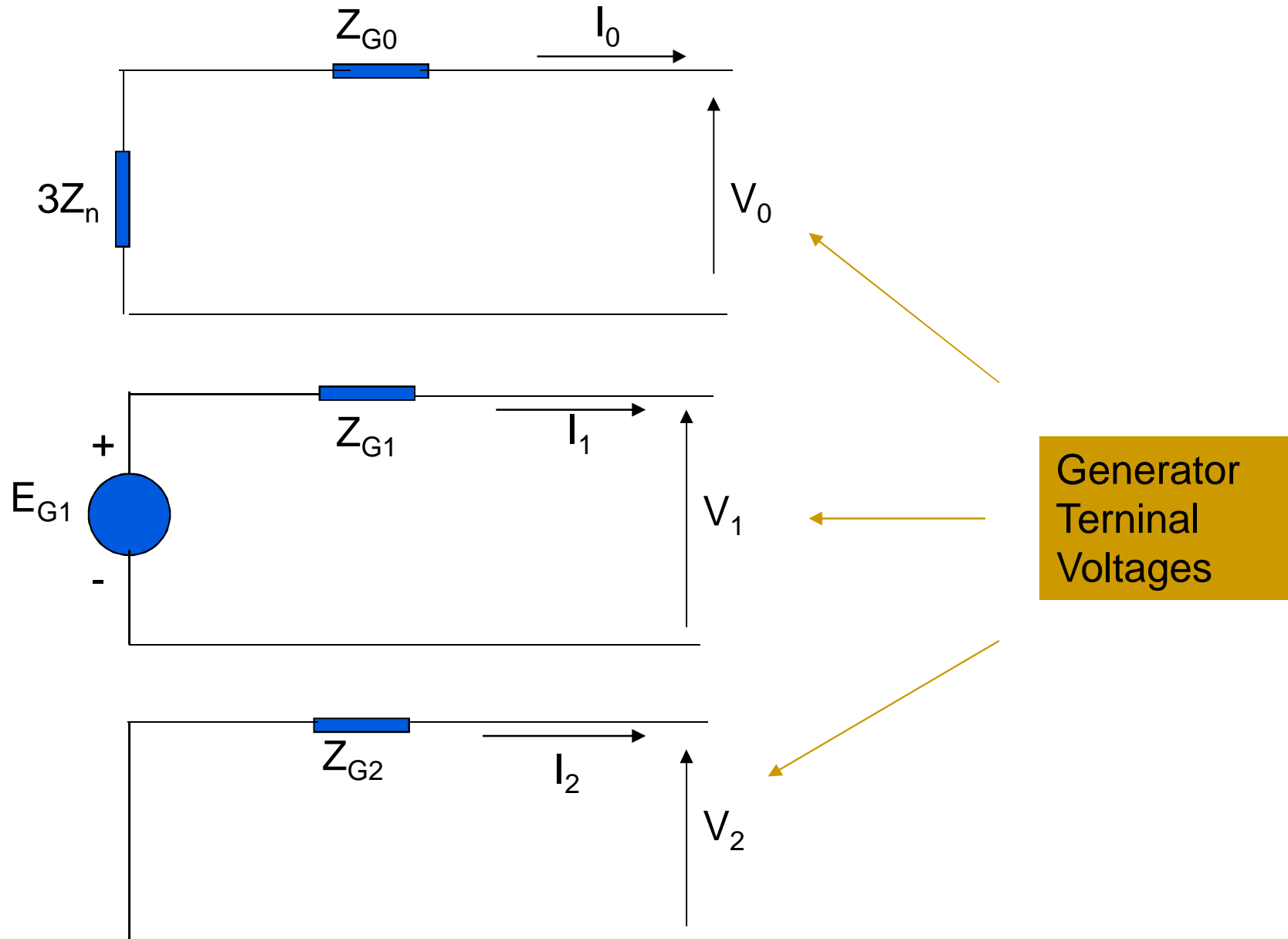
# Rotating Machine Sequence Networks

- Generator sequence circuits are uncoupled



# Symmetrical Components– Gen Constants
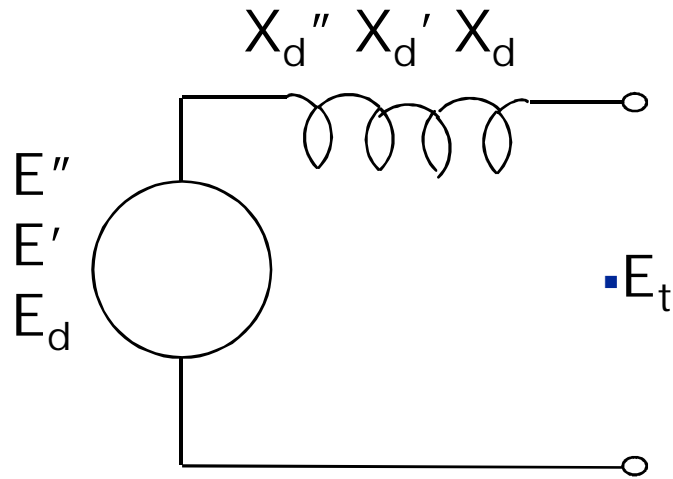
## Internal Machine Voltages and Reactances



$X_d''$  - Subtransient Reactance

$X_d'$  - Transient Reactance

$X_d$  - Synchronous Reactance

# Example Problem


A Generator is connected to a power system through a 22kV delta to 230kV grounded wye transformer rated at 100MVA and with a series reactance of 0.14pu. The generator is rated at 100MVA and 22kV and has  $X''_d = X_2 = 0.16\text{pu}$ . The generator neutral is not grounded. A bolted single line to ground fault occurs at 50 miles down the line on the 230kV terminals of the transformer on Phase A. Assume transmission line is the same 2156KCM Bluebird conductor and arrangement, which was evaluated earlier

## Find:

The fault current in Phase a, b, and c in pu and primary current

The phase voltages at the point of the fault in pu and primary voltage

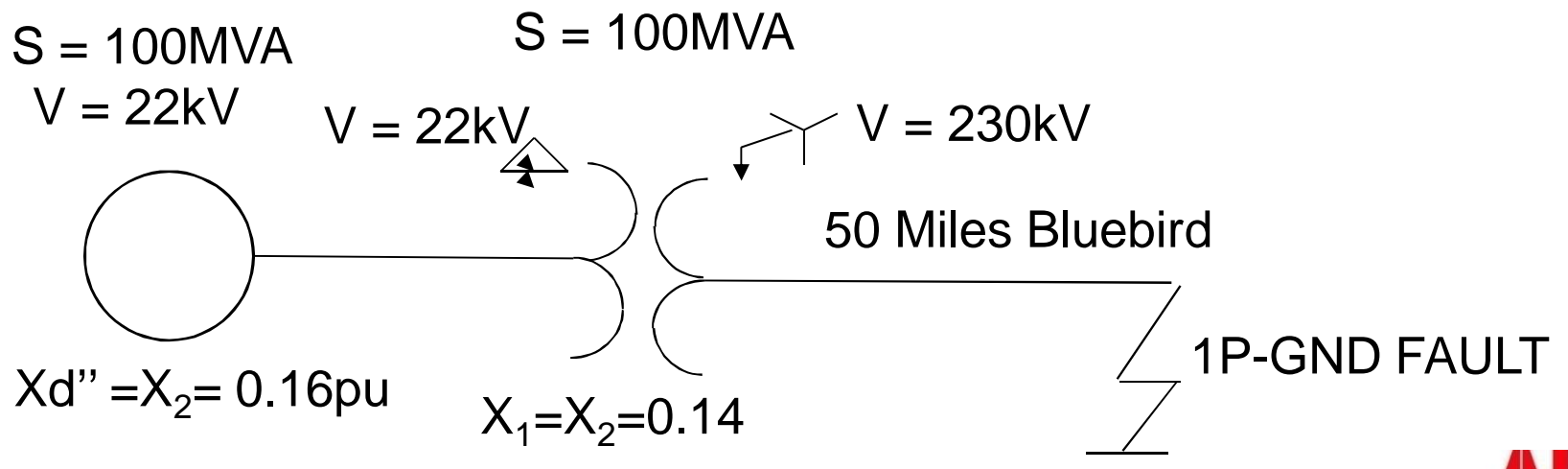
The fault current in Phase a, b, and c in pu and primary current on 22kV side



# Example Problem

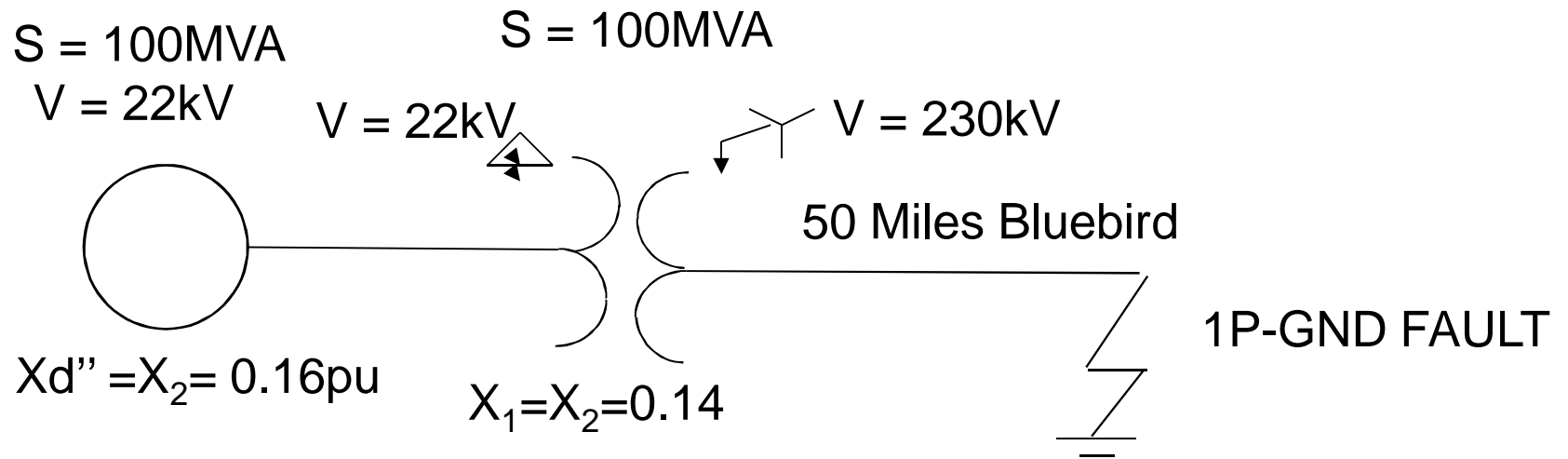**Find:**

The fault current in Phase a, b, and c in pu and primary values



Found earlier that Bluebird conductor characteristics at 60Hz was


$$r_1 = \frac{.0515}{2} = .0258\Omega / mi$$

$$x_1 = .1213 \ln \frac{37.8}{.296} \Omega / mi$$

# Example Problem

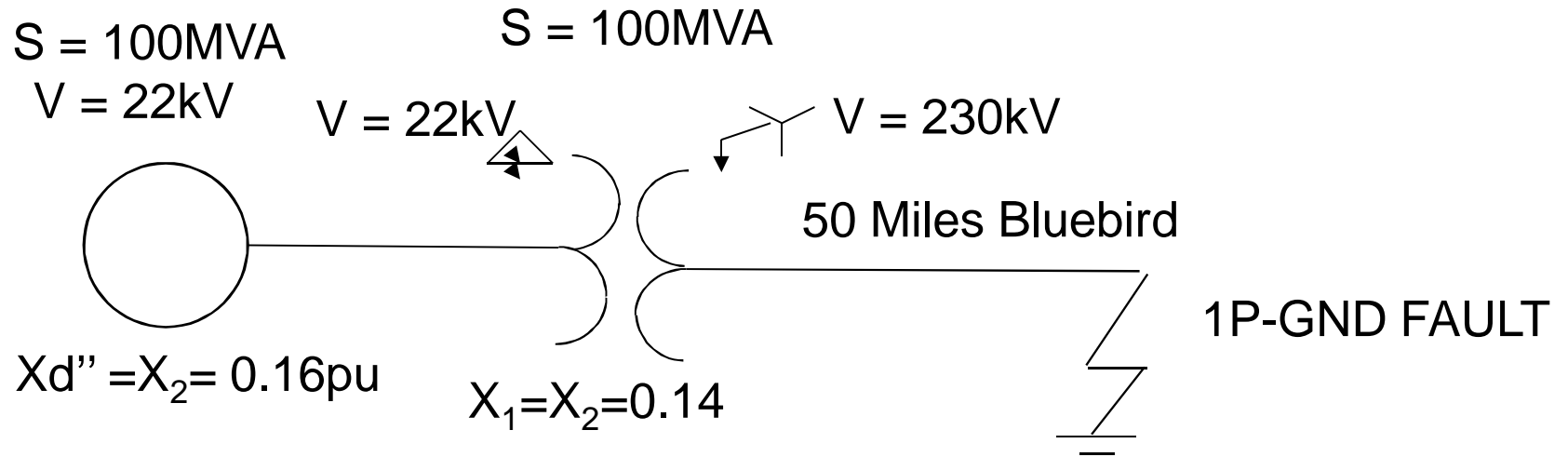**Find:**

The fault current in Phase a, b, and c in pu and primary values



$$Z_{50\text{MILES}} = 50 \times (0.0258 + j0.59)\Omega$$


$$Z_{\text{BASE}} = \frac{kV_{\text{BASE}}^2}{\text{MVA}_{\text{BASE}}} = \frac{230^2}{100} = 529\Omega$$

$$Z_{\text{PU } 50\text{MILES}} = \frac{1.29 + j29.41\Omega}{529} = 0.056 \angle 87.5^\circ \text{ pu}$$


# Example Problem

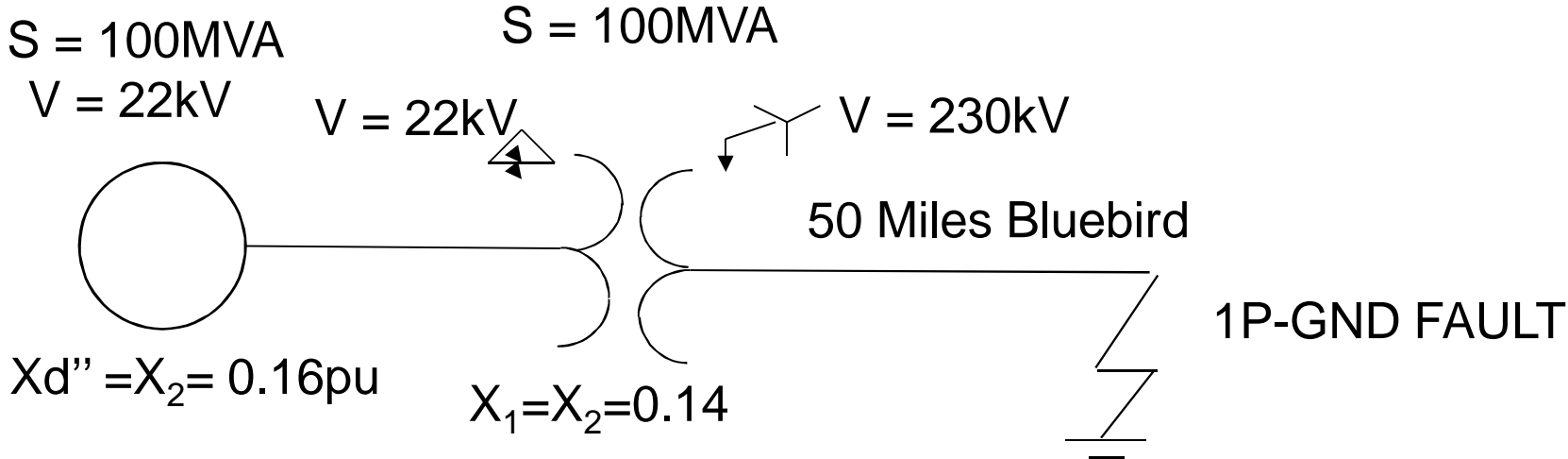**Find:**

The fault current in Phase a, b, and c in pu and primary values



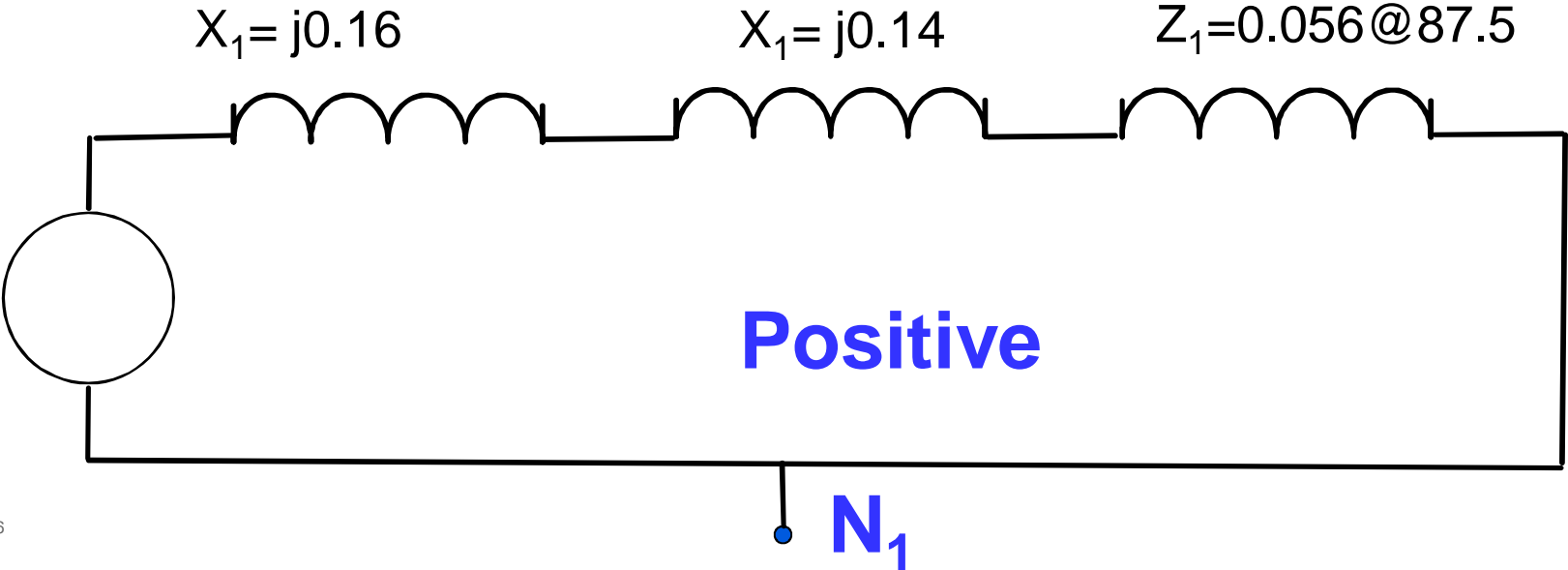
Create our Positive and Negative Sequence networks




# Example Problem

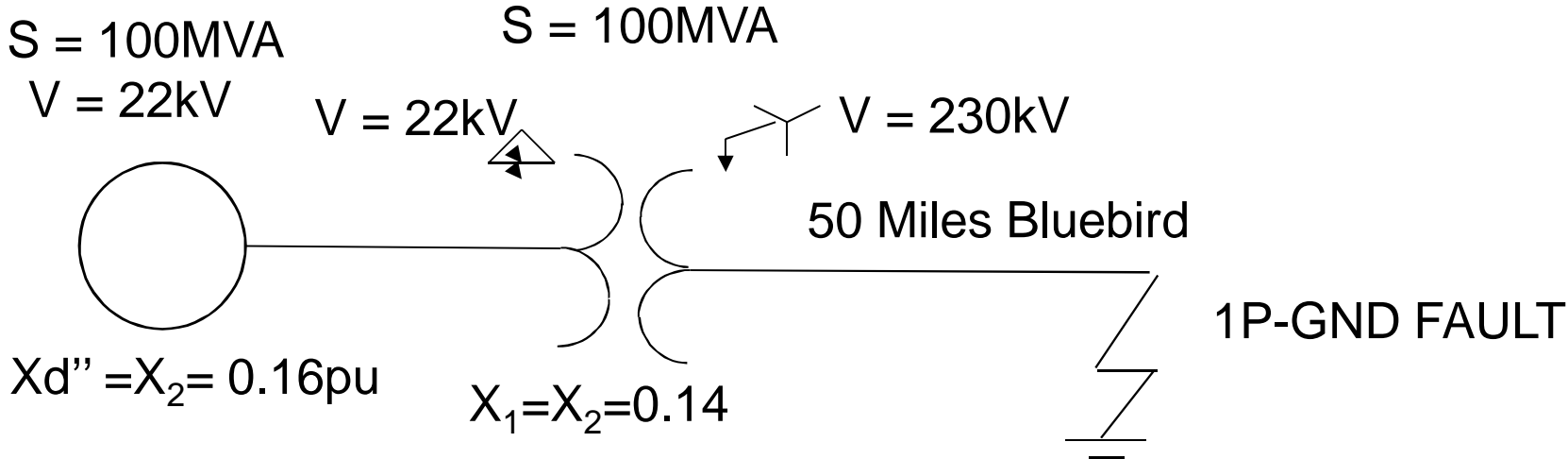**Find:**

The fault current in Phase a, b, and c in pu and primary values



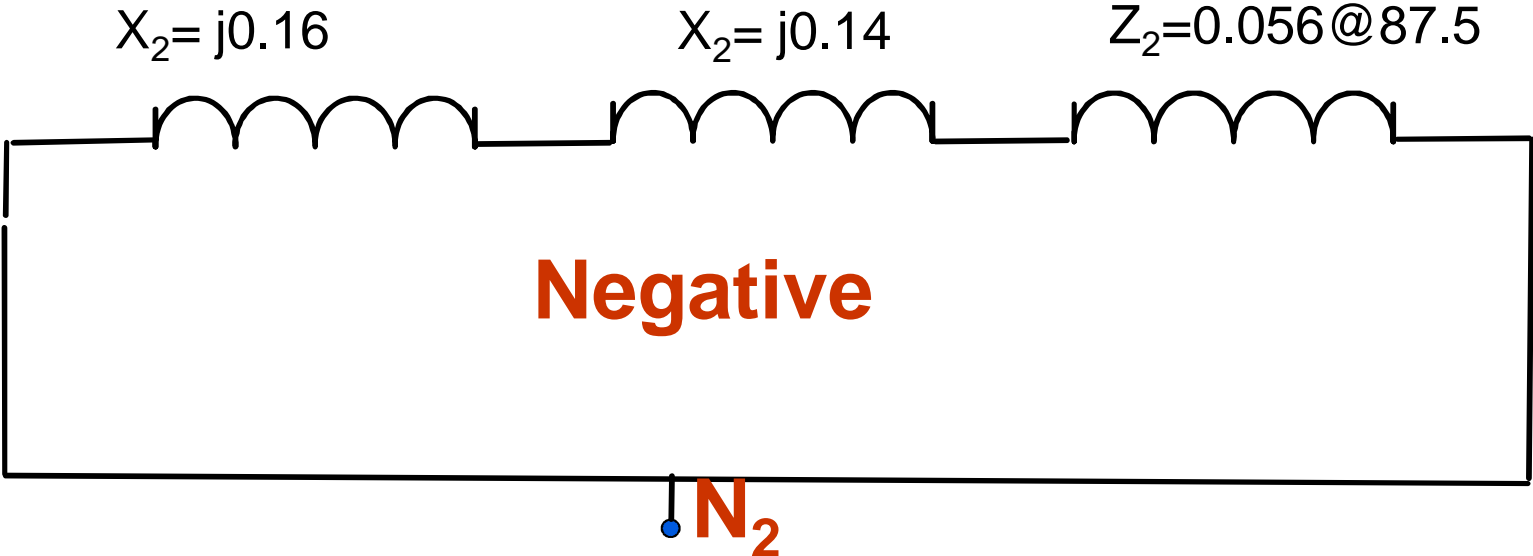Create our Positive and Negative Sequence networks







# Example Problem
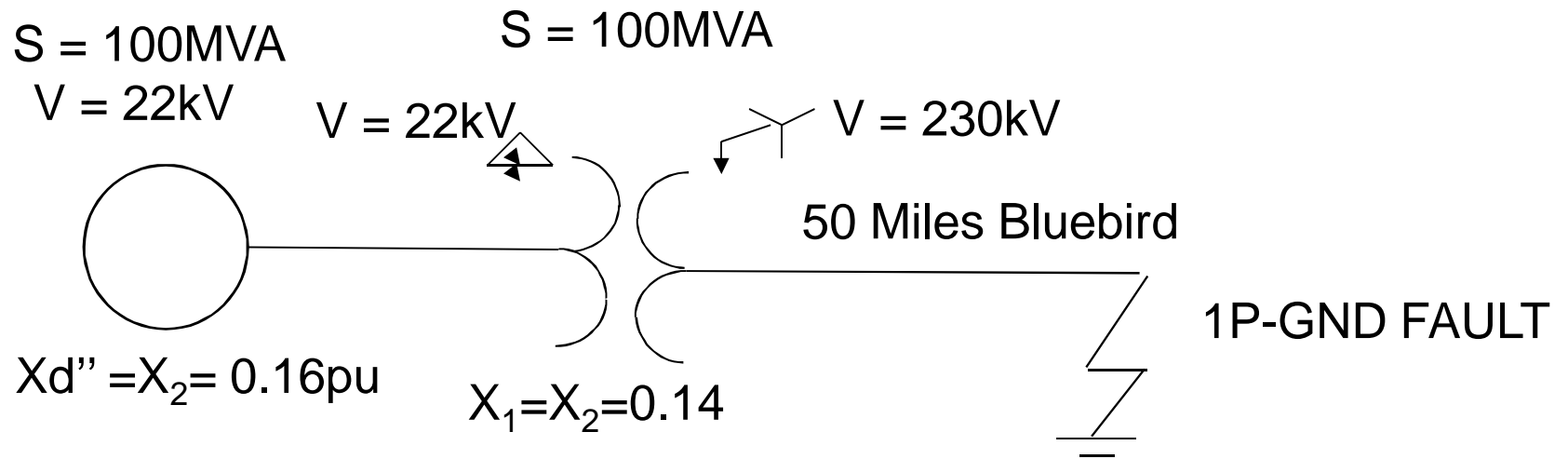
## Find:

The fault current in Phase a, b, and c in pu and primary values



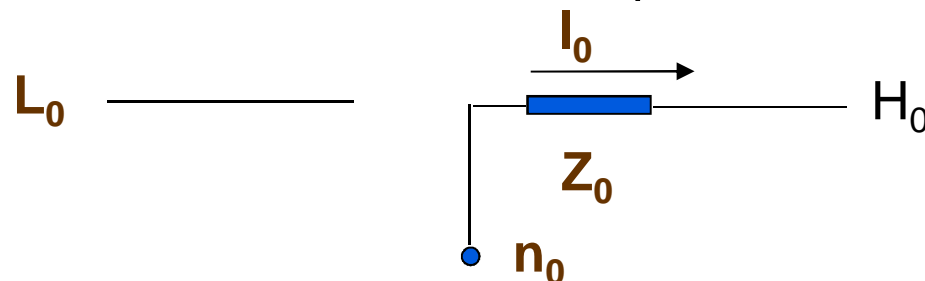
- Create Zero Sequence, For Simplicity Assume  $Z_0 = 3 \times Z_1$  for Transmission Line
- Zero Sequence configuration for a transformer that is delta grounded wye is shown once again below.
- Remembering this we Can Draw the Zero Sequence network for this problem



# Example Problem

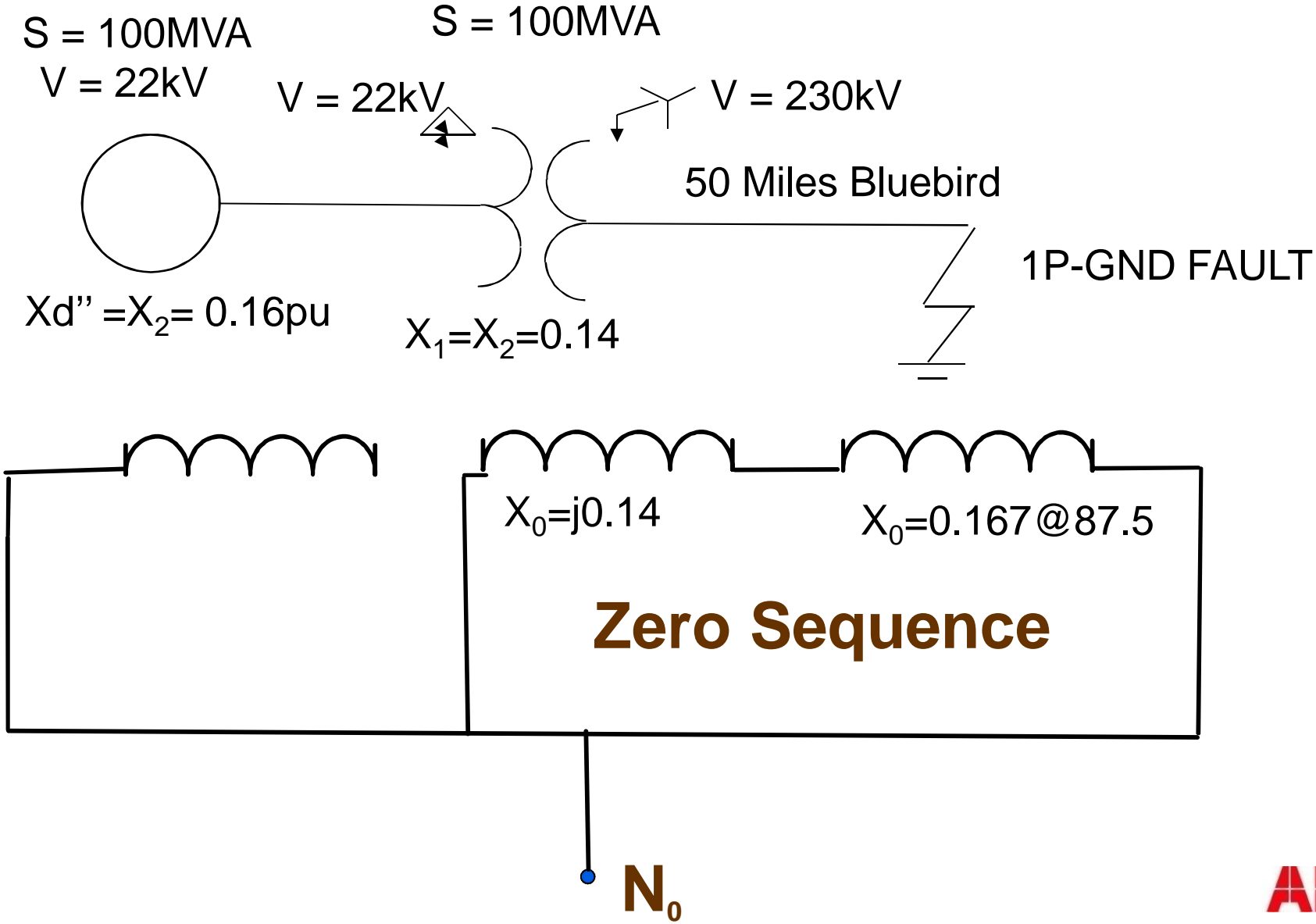**Find:**


The fault current in Phase a, b, and c in pu and primary values




# Example Problem

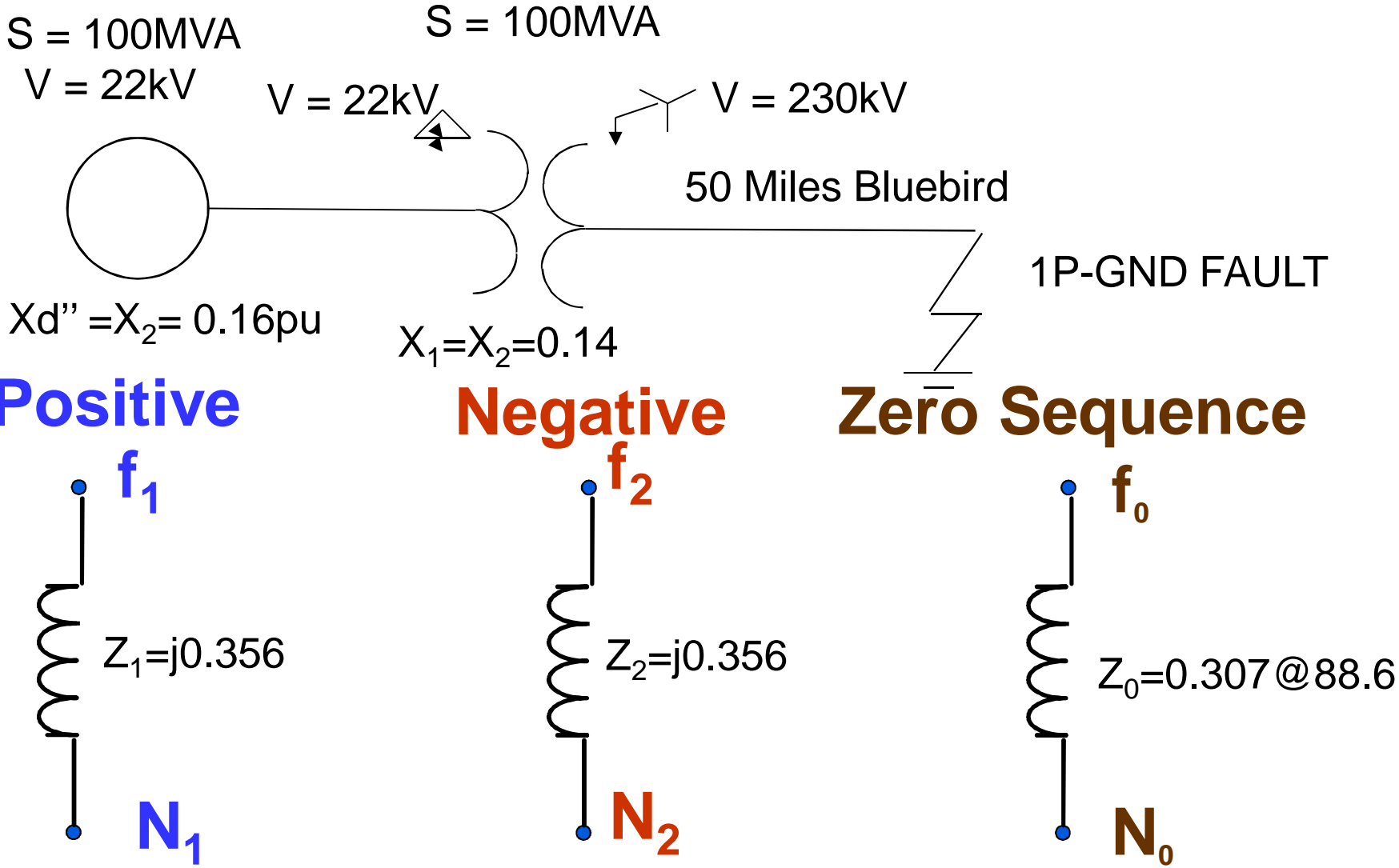**Find:**

The fault current in Phase a, b, and c in pu and primary values



# Example Problem

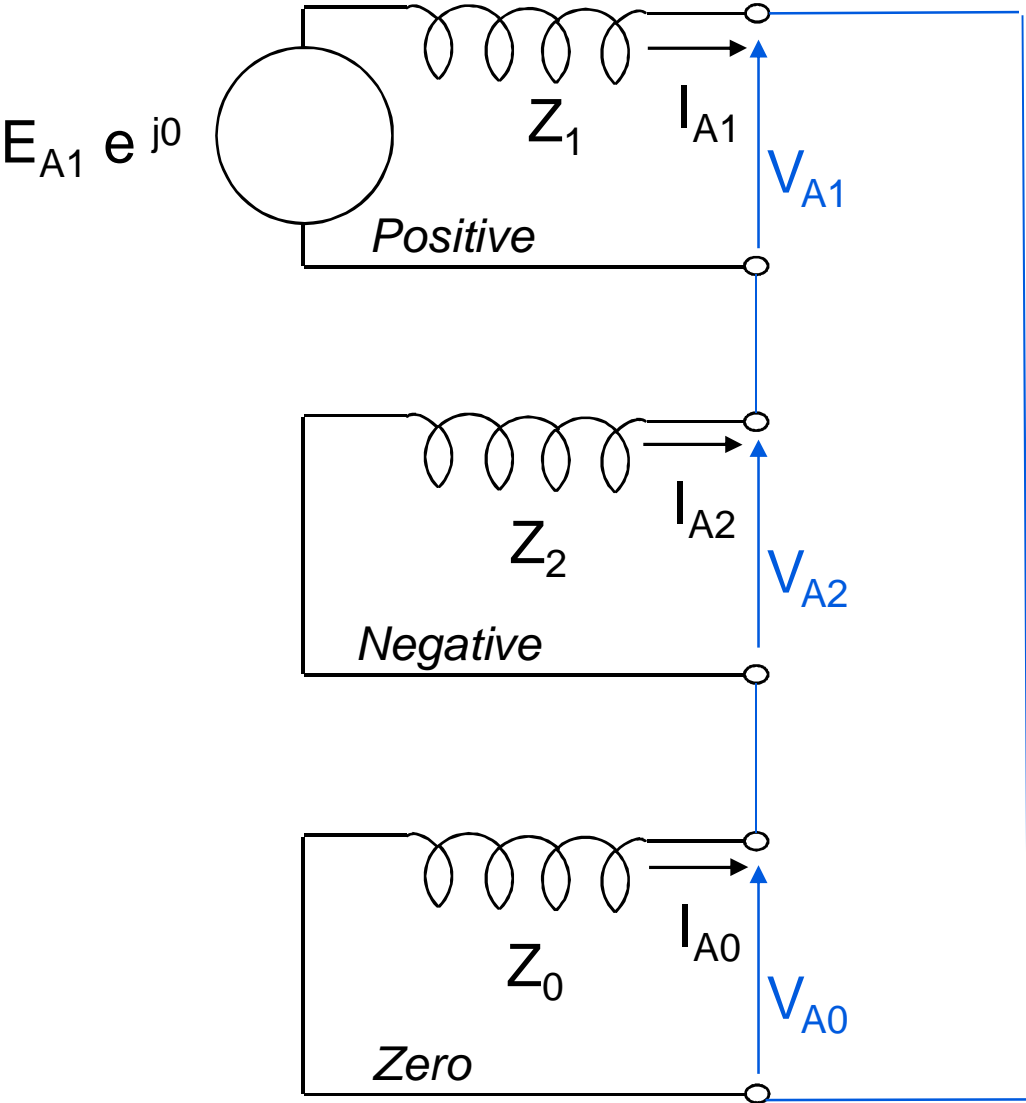

$$I_{PU} = \frac{V_{PU}}{Z_{PU}} = \frac{1 \angle 0^\circ}{j0.356 + j0.356 + 0.307 \angle 88.7^\circ}$$

$$I_{PU} = 1 \angle -89.6^\circ \text{ pu}$$


$$[\mathbf{I}_P] = [\mathbf{A}][\mathbf{I}_S]$$

$$[\mathbf{I}_P] = \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \begin{pmatrix} -j1 \\ -j1 \\ -j1 \end{pmatrix}$$

$$[\mathbf{I}_P] = \begin{pmatrix} -j3 \\ 0 \\ 0 \end{pmatrix} \begin{matrix} A \\ B \\ C \end{matrix} \text{ pu}$$



# Example Problem

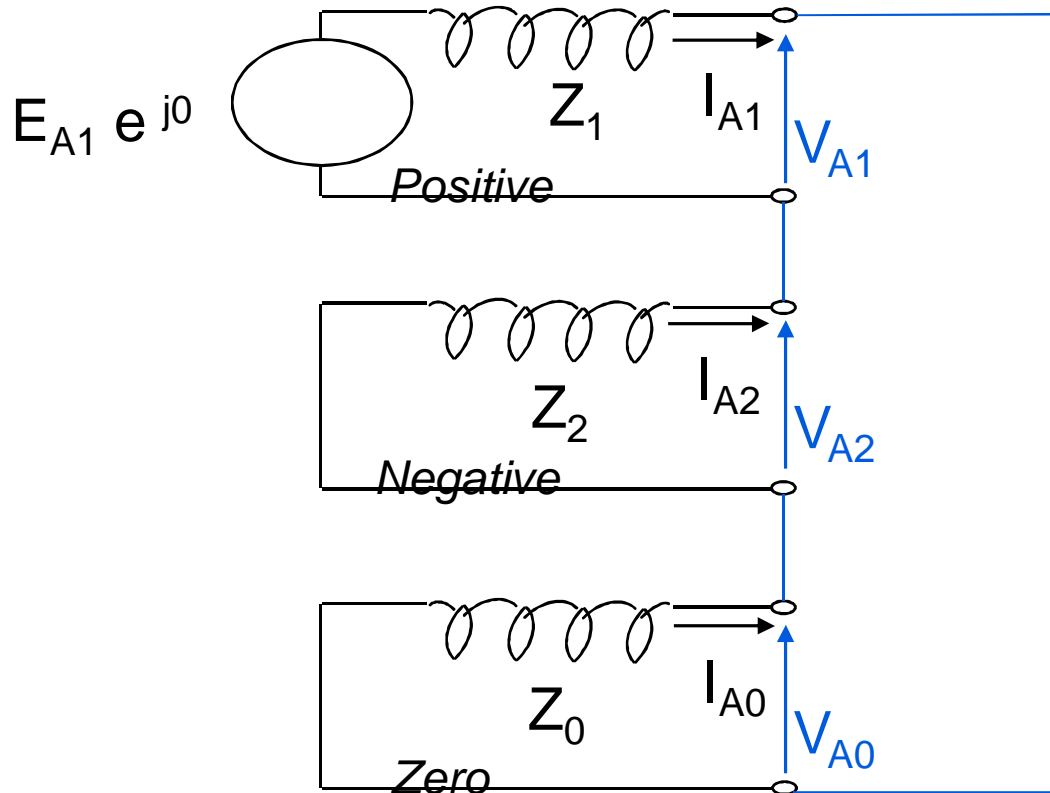

$$I_{BASE} = \frac{S_{BASE}}{\sqrt{3}V_{BASE}} = \frac{100 \times 10^6}{\sqrt{3} \times 230 \times 10^3} = 251A$$

$$[I_P] = \begin{pmatrix} -j753A \\ 0 \\ 0 \end{pmatrix} \begin{matrix} A \\ B \\ C \end{matrix} \text{ Actual}$$

The phase voltages at the point of the fault

$$\begin{pmatrix} V_0 \\ V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \\ 0 \end{pmatrix} - \begin{pmatrix} j0.307 & 0 & 0 \\ 0 & j0.356 & 0 \\ 0 & 0 & j0.356 \end{pmatrix} \begin{pmatrix} -j1 \\ -j1 \\ -j1 \end{pmatrix} = \begin{pmatrix} -0.307 \\ 0.644 \\ -0.356 \end{pmatrix}$$

# Example Problem

The phase voltages at the point of the fault

$$\begin{pmatrix} V_0 \\ V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \\ 0 \end{pmatrix} - \begin{pmatrix} j0.307 & 0 & 0 \\ 0 & j0.356 & 0 \\ 0 & 0 & j0.356 \end{pmatrix} \begin{pmatrix} -j1 \\ -j1 \\ -j1 \end{pmatrix} = \begin{pmatrix} -0.307 \\ 0.644 \\ -0.356 \end{pmatrix}$$


$$[\mathbf{V}_P] = [\mathbf{A}][\mathbf{V}_S]$$

$$[\mathbf{V}_P] = \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \begin{pmatrix} -0.307 \\ 0.644 \\ -0.356 \end{pmatrix} = \begin{pmatrix} 0 \\ 0.976@-117.5 \\ 0.976@117.5 \end{pmatrix} \quad \text{pu}$$


$$V_{PHASE} = V_{BASE} \times V_{PU}$$

$$[\mathbf{V}_P] = \begin{pmatrix} 0 \\ 224.5@-87.5 \text{ kV} \\ 224.5@147.5 \text{ kV} \end{pmatrix} \begin{matrix} \text{A} \\ \text{B} \\ \text{C} \end{matrix} \quad \text{Actual}$$

# Phase-to-ground Fault

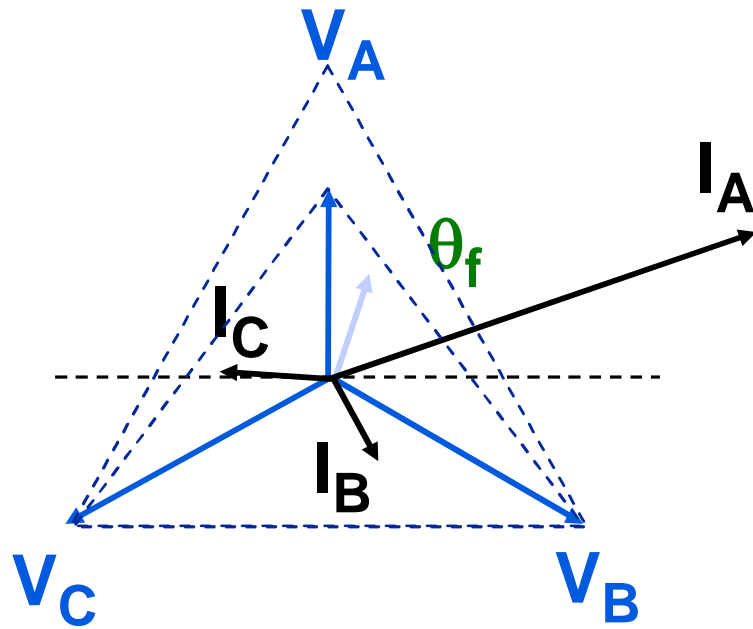


Phase Quantities

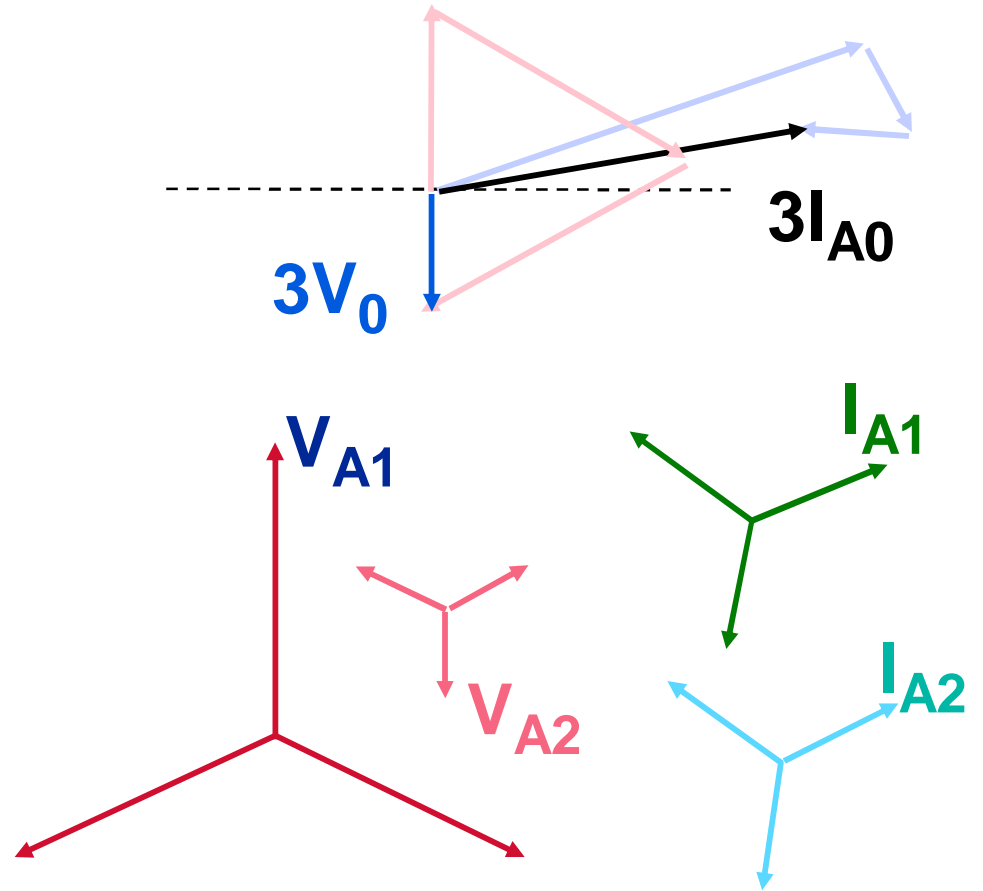

Symmetrical Components

# Phase-to-ground Fault Voltage Profile

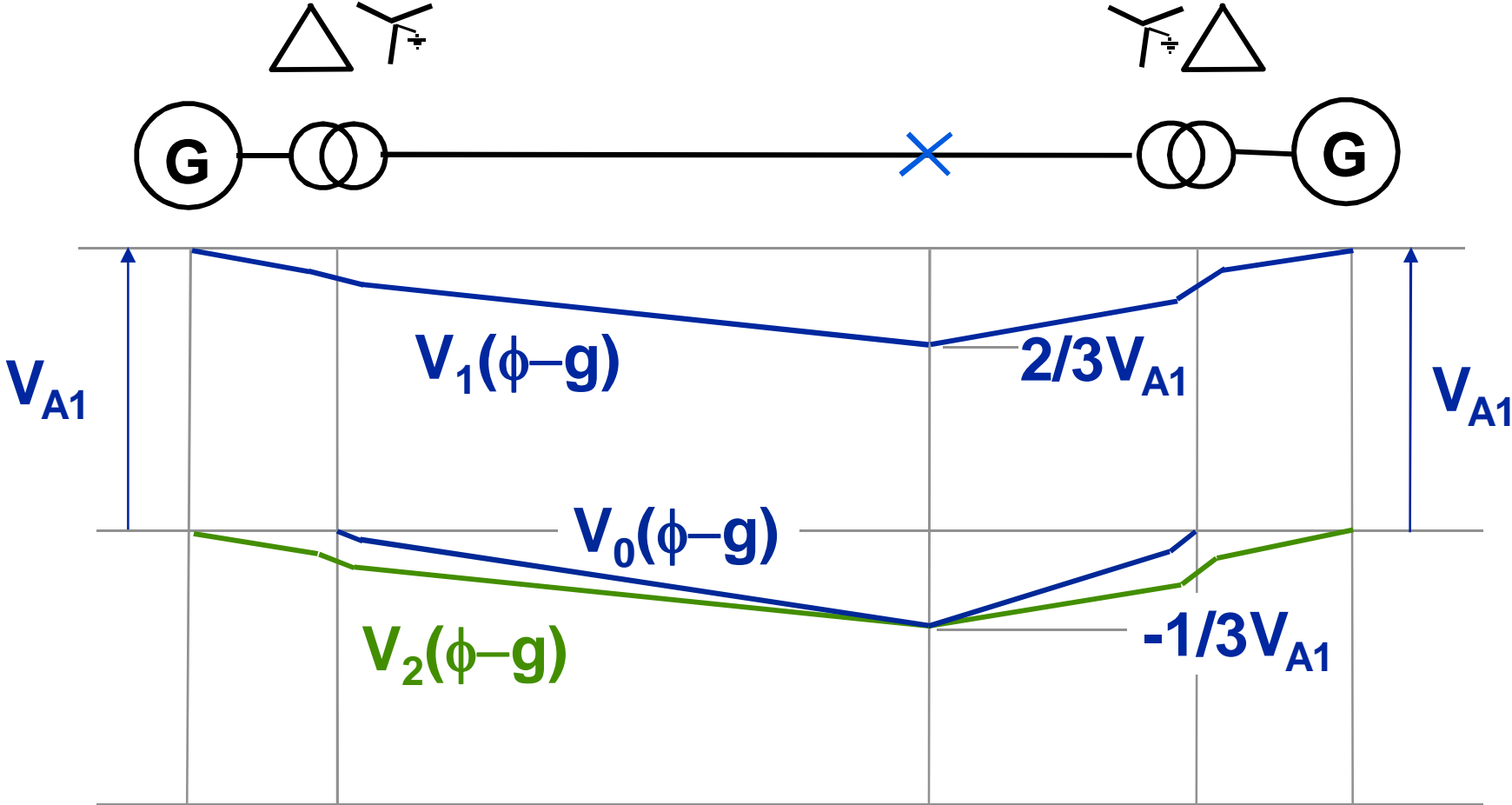


These magnitudes assume  $Z_1 = Z_2 = Z_0$


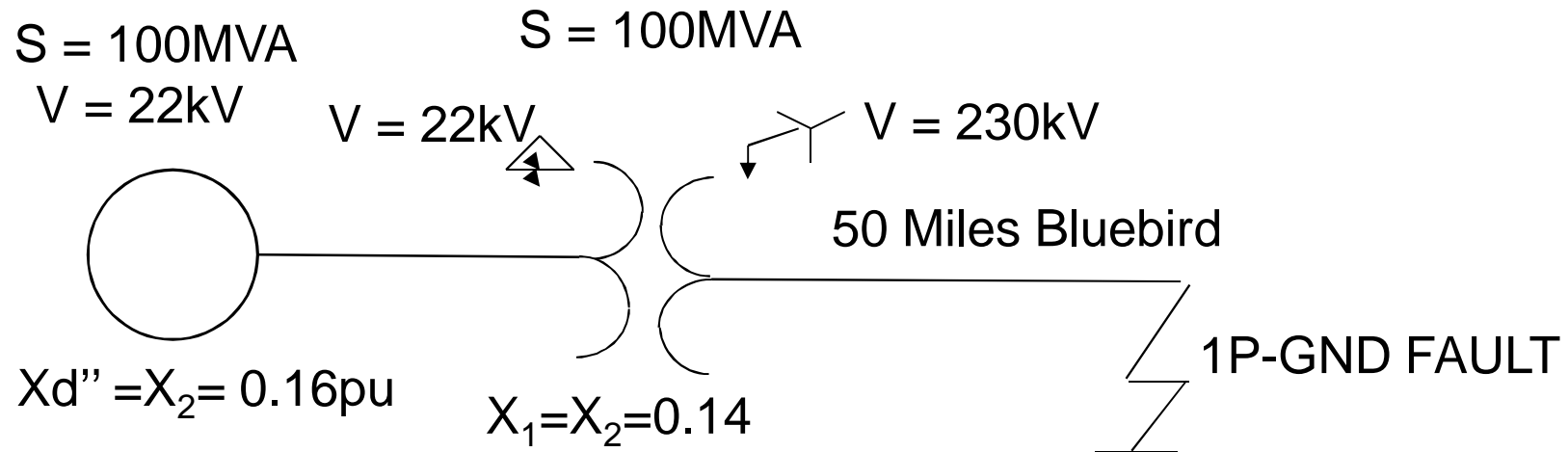
# Example Problem

The fault current in Phase a, b, and c in pu and primary current on 22kV side



Found Earlier our phase and sequence quantities in pu on the 230kV side of Transformer


$$[\mathbf{I}_p] = [\mathbf{A}][\mathbf{I}_s]$$

$$[\mathbf{I}_{\text{Sprimary}}] = \begin{pmatrix} -j1 \\ -j1 \\ -j1 \end{pmatrix} \begin{matrix} \text{Zero} \\ \text{Positive} \\ \text{Negative} \end{matrix}$$

Knowing this information we can find Phase currents on the 22kV side of Transformer
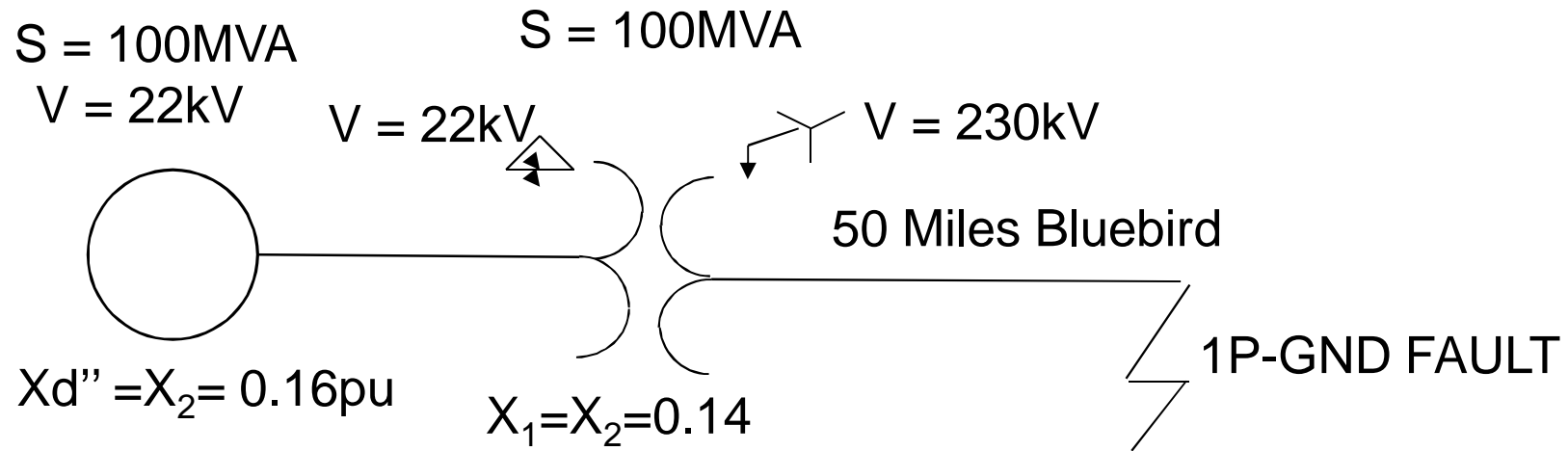
# Example Problem

The fault current in Phase a, b, and c in pu and primary current on 22kV side




Looking back Zero Sequence current has no path to flow on the 22kV side

$$[\mathbf{I}_{\text{Secondary}}] = \begin{pmatrix} 0 \\ 1 @ -120 \\ 1 @ -60 \end{pmatrix} \begin{matrix} \text{Zero} \\ \text{Positive} \\ \text{Negative} \end{matrix}$$

How do these differ from currents on the 230kV side?
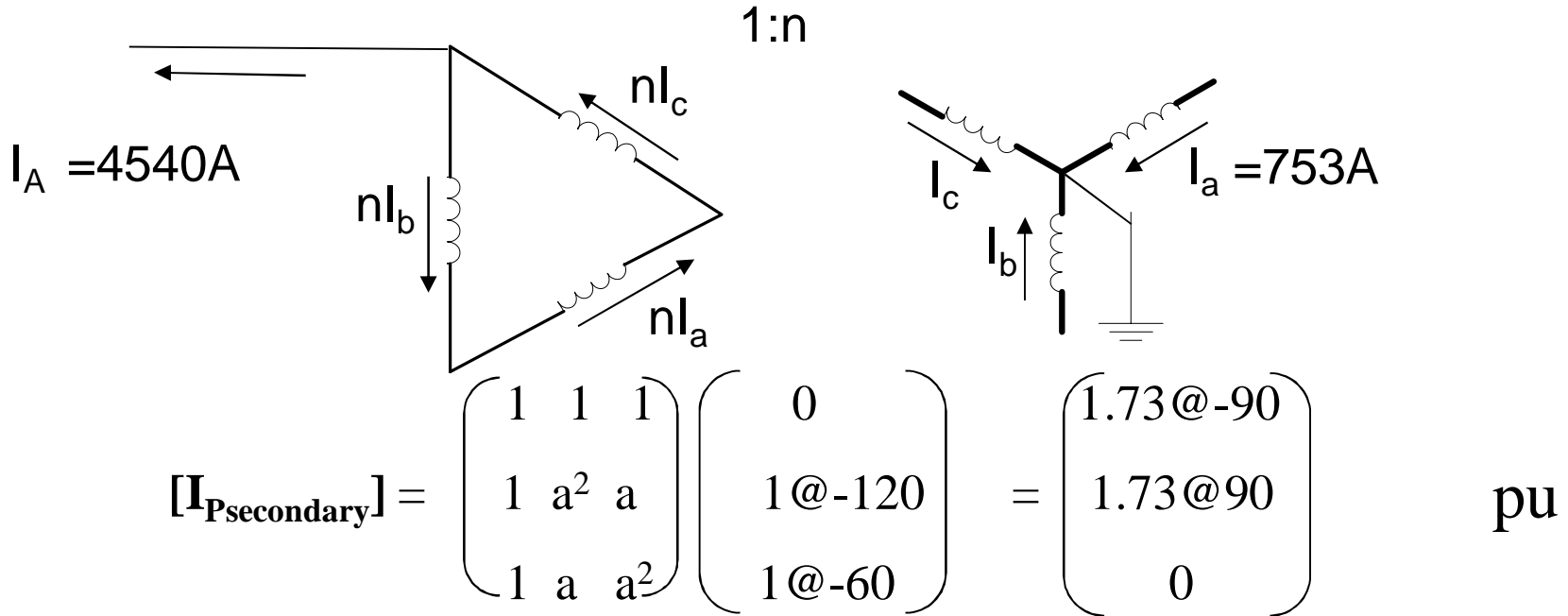
# Example Problem

The fault current in Phase a, b, and c in pu and primary current on 22kV side




$$I_{\text{sec\_act}} = \frac{753 \times \frac{220\text{kV}}{22\text{kV}}}{\sqrt{3}} = 4540$$

$$I_{\text{base}} = \frac{S_{\text{BASE}}}{\sqrt{3} \times V_{\text{BASE}}} = \frac{100 \times 10^6}{\sqrt{3} \times 22 \times 10^3} = 2624 \text{ A}$$

$$[\mathbf{I}_{\text{Psecondary}}] = \begin{pmatrix} -j4540 \text{ A} \\ j4540 \text{ A} \\ 0 \end{pmatrix} \begin{matrix} \text{A} \\ \text{B} \\ \text{C} \end{matrix} \quad \text{Actual}$$
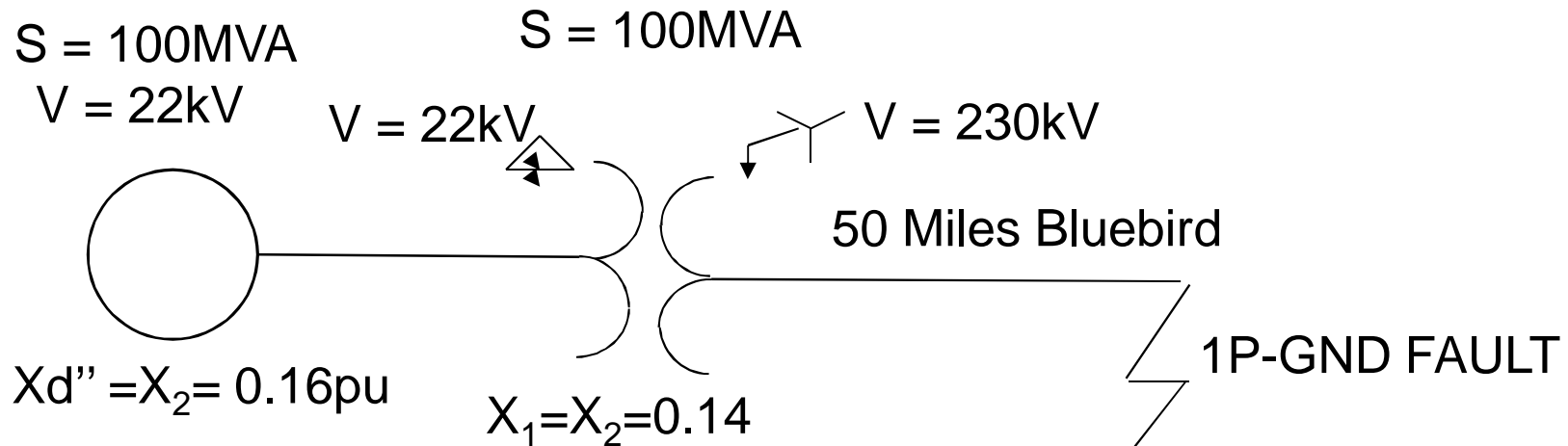
# Example Problem

The fault current in Phase a, b, and c in pu and primary current on 22kV side




$$[\mathbf{I}_{\text{Pprimary}}] = \begin{pmatrix} -j753\text{A} \\ 0 \\ 0 \end{pmatrix} \begin{matrix} \text{A} \\ \text{B} \\ \text{C} \end{matrix} \quad \text{Actual}$$


$$[\mathbf{I}_{\text{Psecondary}}] = \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \begin{pmatrix} 0 \\ 1@-120 \\ 1@-60 \end{pmatrix} = \begin{pmatrix} 4540@-90 \\ 4540@90 \\ 0 \end{pmatrix} \quad \text{Actual}$$

What has this taught us?

# Phase-to-phase Fault

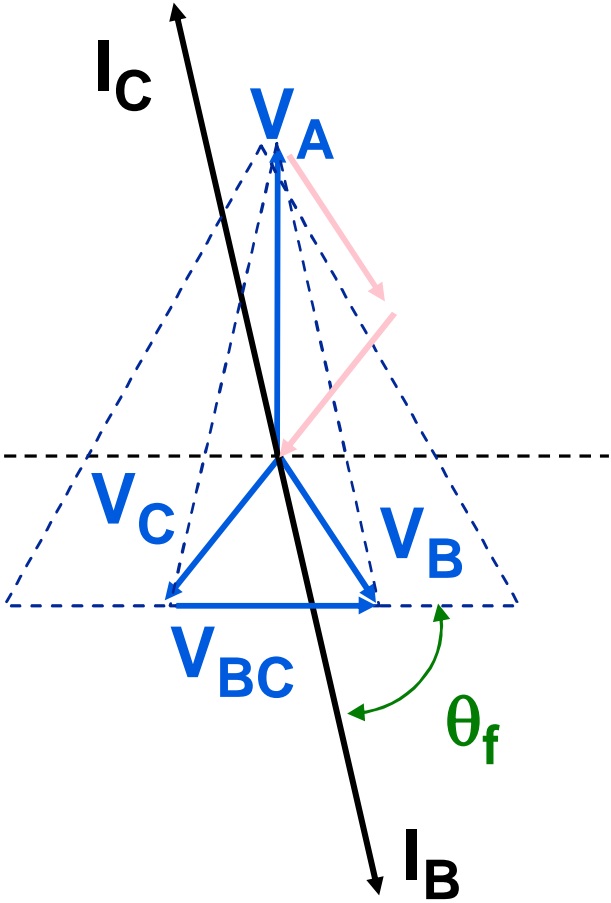


Phase Quantities

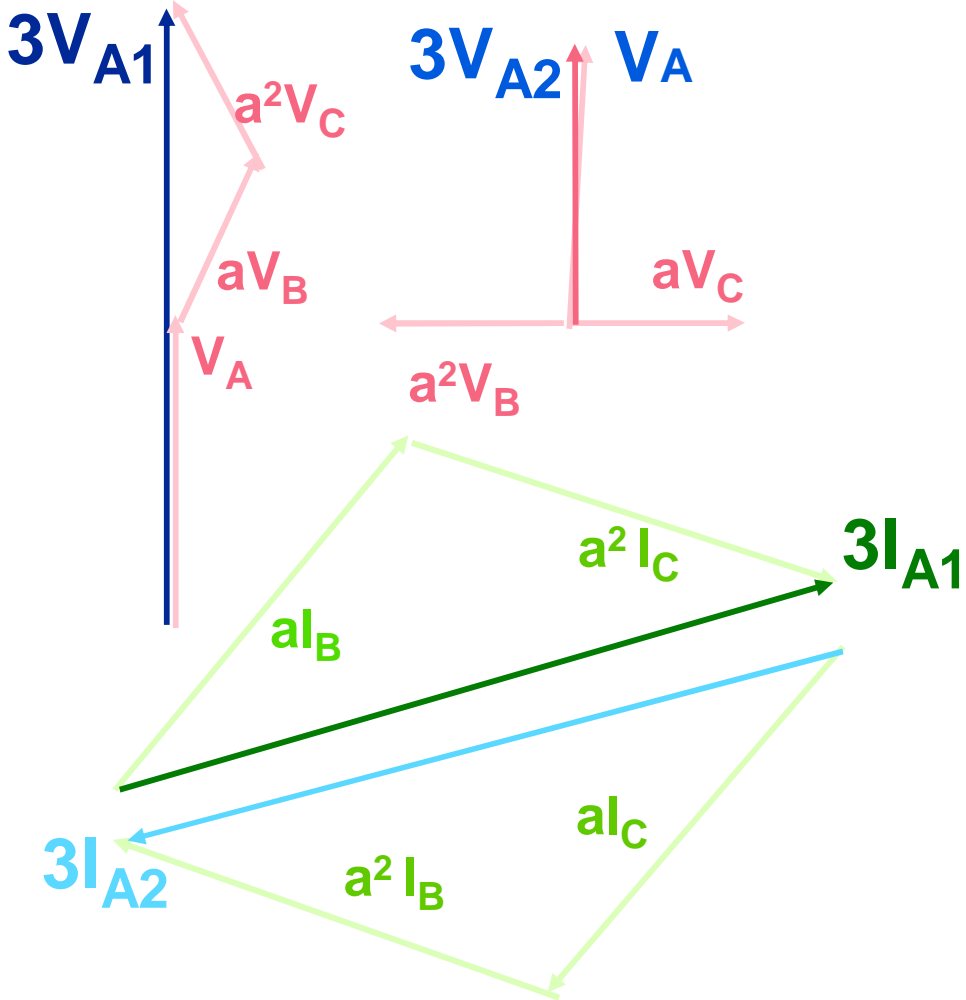

Symmetrical Components

# Waveforms from SLG fault

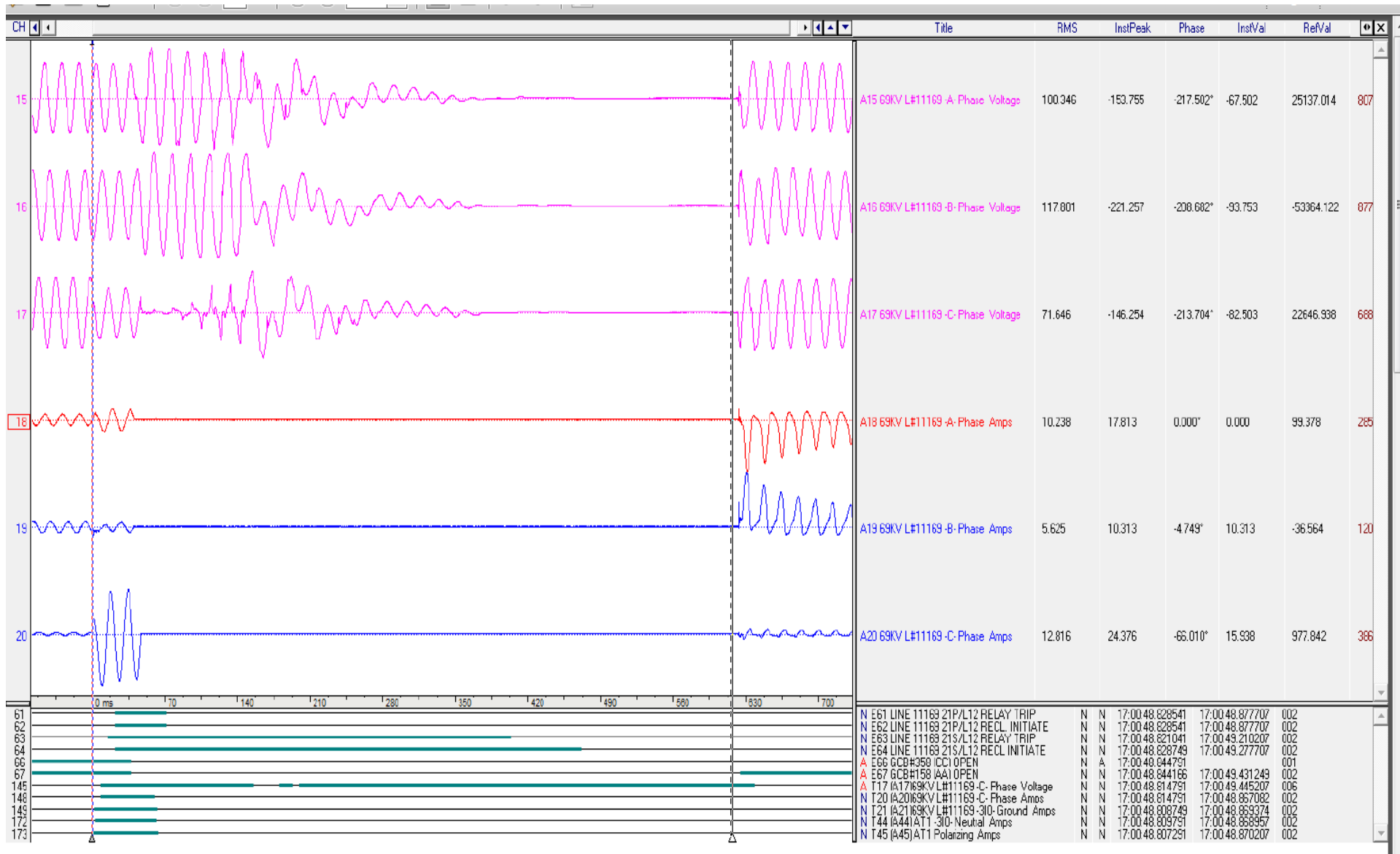

# Symmetrical Components Learned Objectives

- What we will discuss
  - Overview of converting phase quantities to symmetrical quantities and symmetrical to phase
  - Sequence Impedance networks – How do we build one?
  - Evaluating a Impedance network – Example Problem
  - Insights into the Example Problem
- Why do we use this method?
  - Not using it would require writing loop equations for the system and solving. – For simple systems it's not an easy task
  - To date it is still the only real practical solution to problems of unbalanced electrical circuits.

Power and productivity  
for a better world™





# Thank you for your participation

Shortly, you will receive a link to an archive of this presentation. To view a schedule of remaining webinars in this series, or for more information on ABB's protection and control solutions, visit:

**[www.abb.com/relion](http://www.abb.com/relion)**